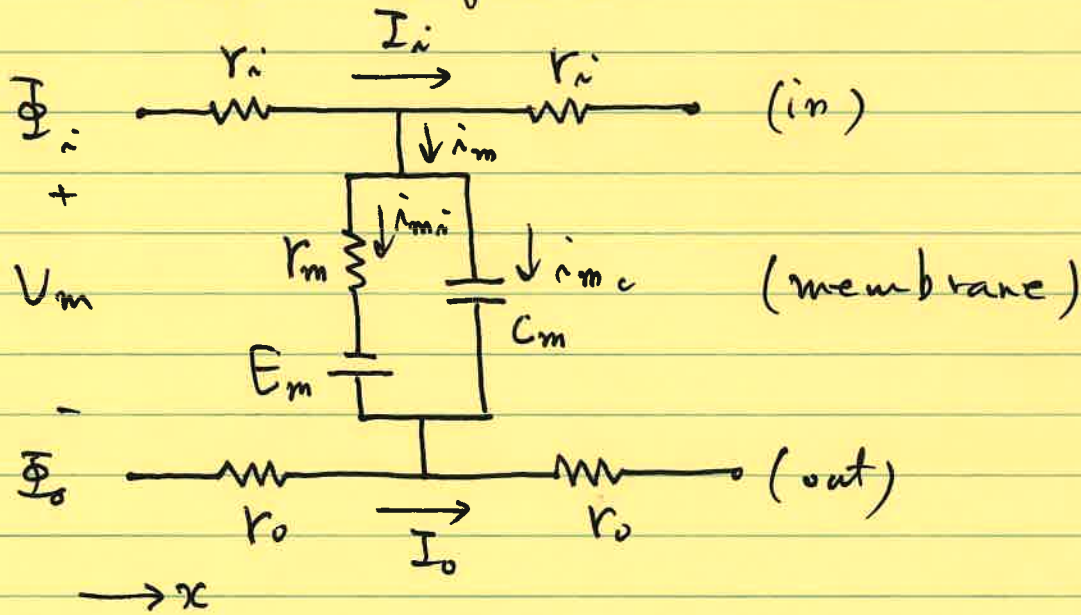


# \* Cable Equation

(1)



$r_i$  : intracellular axial resistance  
 per unit length ( $\Omega/m$ )  
 $r_o$  : extracellular " ( $\Omega/m$ )  
 times unit length  
 $r_m$  : membrane resistance ( $\Omega \cdot m$ )  
 in radial direction  
 $C_m$  : membrane capacitance per unit  
 length (F/m)

$I_i$  : total longitudinal intracellular  
 current (A)

$I_o$  : " " extracellular  
 (A)

$i_m$  : total transmembrane current  
 per unit length (A/m)

$i_{mc}$  : capacitive component of  $i_m$

$i_{mi}$  : ionic "

(2)

$\Phi_i$  : potential inside membrane [V]

$\Phi_o$  : " outside " [V]

$V_m = \Phi_i - \Phi_o$  : membrane voltage [V]

$V_r$  : resting membrane voltage [V]

$V' = V_m - V_r$  : deviation of membrane voltage from  $V_r$

Without stimulating current,  $I_i + I_o = 0$

At resting state,  $I_i = I_o = I_m = 0$ ,  $V_m = V_r$ ,  $V' = 0$

During activation,  $I_i + I_o = 0$ ,  $V' \neq 0$

Since  $V_r$  is constant for all  $x$ ,

$$\frac{\partial V'}{\partial x} = \frac{\partial V_m}{\partial x}, \quad \frac{\partial V'}{\partial t} = \frac{\partial V_m}{\partial t}$$

② In steady state,  $\frac{\partial}{\partial t} = 0$

$$\frac{\partial \Phi_i}{\partial x} = -I_i r_i, \quad \frac{\partial \Phi_o}{\partial x} = -I_o r_o$$

$$\dot{\lambda}_{m} = -\frac{\partial I_i}{\partial x} = \frac{\partial I_o}{\partial x}$$

(loss of  $I_i$ ) (gain of  $I_o$ )

$$\frac{\partial V'}{\partial x} = \frac{\partial \Phi_i}{\partial x} - \frac{\partial \Phi_o}{\partial x} = -I_i r_i + I_o r_o \quad (3)$$

$$\frac{\partial^2 V'}{\partial x^2} = -r_i \underbrace{\frac{\partial I_i}{\partial x}}_{-i_m} + r_o \underbrace{\frac{\partial I_o}{\partial x}}_{i_m} = (r_i + r_o) i_m$$


Since  $C_m \frac{dV'_o}{dt} = 0$ ,  $i_m = \frac{V'}{r_m}$

$$\frac{\partial^2 V'}{\partial x^2} = \frac{r_i + r_o}{r_m} V'$$

$$\frac{\partial^2 V'}{\partial x^2} - \lambda^2 V' = 0, \quad \lambda = \sqrt{\frac{r_m}{r_i + r_o}} \approx \sqrt{\frac{r_m}{r_i}}$$

$$V'_{x=0} = V'(0), \quad V'_{x=\infty} = 0$$

$$V'(x) = V'(0) e^{-\frac{x}{\lambda}}$$

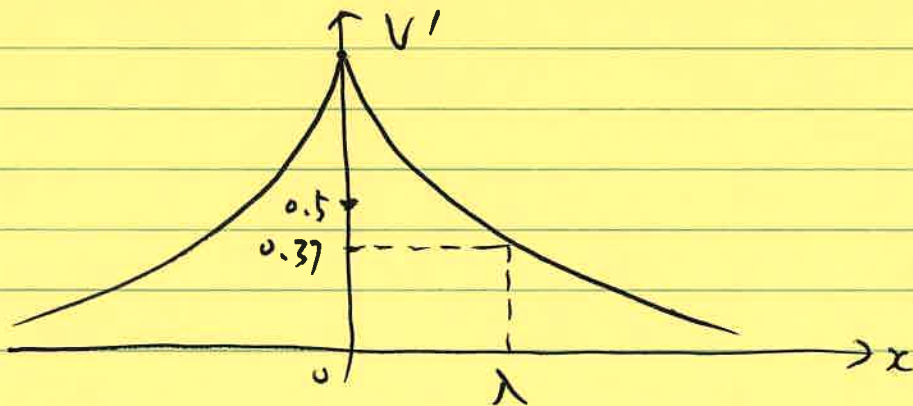

④

② Step-current stimulation

$$\dot{I}_m = \dot{I}_{m_i} + \dot{I}_{m_e}$$

$$\frac{I}{r_i + r_o} \frac{\partial^2 V'}{\partial x^2} = \frac{V'}{r_m} + C_m \frac{\partial V'}{\partial t}$$

$$\frac{r_m}{r_i + r_o} \frac{\partial^2 V'}{\partial x^2} - V' - r_m C_m \frac{\partial V'}{\partial t} = 0$$

$$-\lambda^2 \frac{\partial^2 V'}{\partial x^2} + \tau \frac{\partial V'}{\partial t} + V' = 0$$