

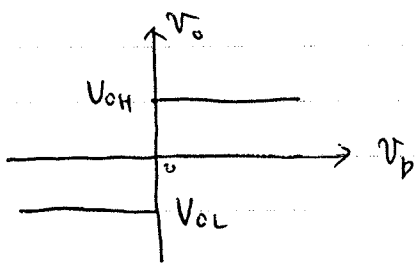


# Chapter 9 Nonlinear Circuits

## 9.1 Voltage Comparators

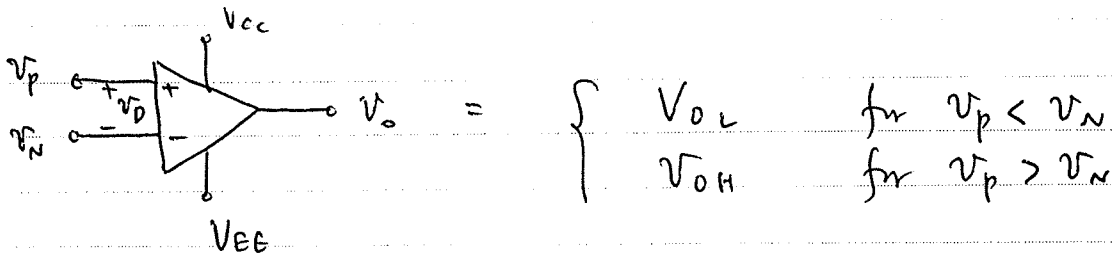


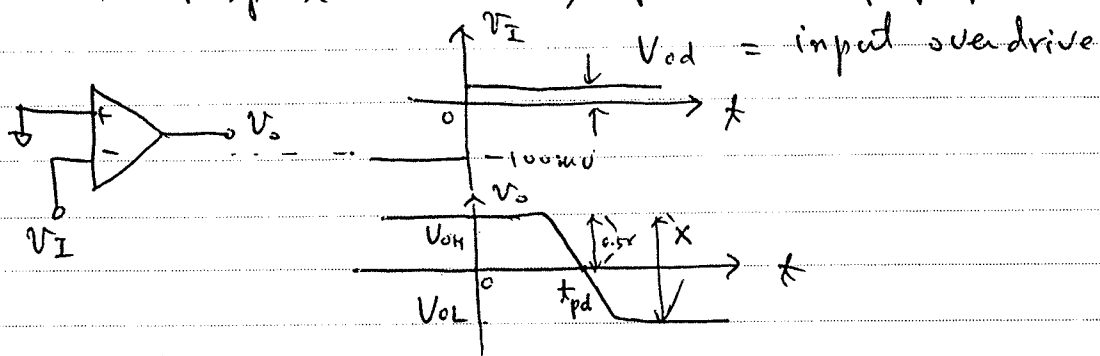
\* Response Time,  $t_{pd}$  (= propagation delay)



\* Threshold Detector : Fig 9.3 (p 403)

\* LM 311 Voltage Comparator : Fig 9.5 (p 405)

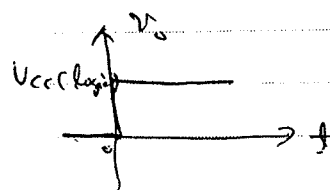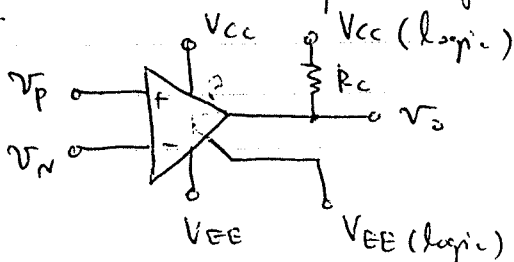$v_p > v_n \Rightarrow \text{out } 0$   
 $v_p < v_n \Rightarrow \text{out } 1$




\* High-Speed Comparator

- CMP-05 (AD)
- LT1016 (LT)

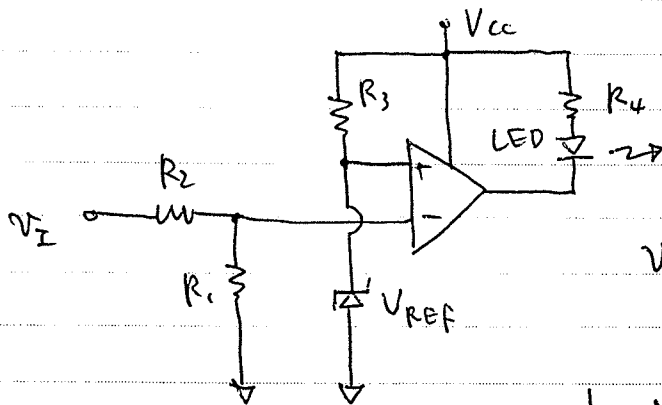9.2 Comparator Applications

\* Level Detector (or Threshold Detector)



$$V_N = \frac{R_1}{R_1 + R_2} V_I$$

at  $V_N = V_T$ ,  $V_N = V_{REF}$

$$\Rightarrow V_T = \left(1 + \frac{R_2}{R_1}\right) V_{REF}$$

- (i)  $V_I < V_T$ , LED off
- (ii)  $V_I > V_T$ , LED ON

\* ON - OFF Control

Fig 9.12 (p 412) : Temp. controller (thermostat)

- LM335 : Temp. sensor

$$V(T) = T/100, T \text{ in kelvin}$$

$\left\{ \begin{array}{l} T \uparrow \rightarrow V_N > V_p \rightarrow Q_0 \text{ ON} \rightarrow \text{LM335 off} \rightarrow \text{Heater off} \\ T \downarrow \rightarrow V_N < V_p \rightarrow Q_0 \text{ OFF} \rightarrow \text{LM335 on} \rightarrow \text{Heater ON} \end{array} \right.$

$T \uparrow \rightarrow V_N > V_p \rightarrow Q_0 \text{ saturate} \rightarrow \text{LM335 off} \rightarrow \text{Heater off}$

$T \downarrow \rightarrow V_N < V_p \rightarrow Q_0 \text{ cut-off} \rightarrow \text{LM335 on} \rightarrow \text{Heater ON}$

$v_I < V_{TL} \rightarrow Q_1 \text{ OFF}, Q_2 \text{ ON} \rightarrow v_o = 0$   
 $V_{TL} < v_I < V_{TH} \rightarrow Q_1 \text{ OFF}, Q_2 \text{ OFF} \rightarrow v_o = V_{CC}$   
 $v_I > V_{TH} \rightarrow Q_1 \text{ ON}, Q_2 \text{ OFF} \rightarrow v_o = 0$

- LM 395 : high-beta power transistor
- LM 329 : 6.9V reference diode

### \* Window Detectors (Window Comparator)

~~$v_I < V_{TL} \rightarrow Q_1 \text{ ON}, Q_2 \text{ OFF} \rightarrow v_o = 0$   
 $V_{TL} < v_I < V_{TH} \rightarrow Q_1 \text{ OFF}, Q_2 \text{ OFF} \rightarrow v_o = V_{CC}$   
 $v_I > V_{TH} \rightarrow Q_1 \text{ ON}, Q_2 \text{ OFF} \rightarrow v_o = 0$~~

- Fig 9.13 (p 413)

- Fig 9.14 (p 413) : application

\* Bar Graph Meters : Fig 9.15 (p 415)

Fig 9.16 (p 416)

### \* Pulse Width Modulation (PWM)


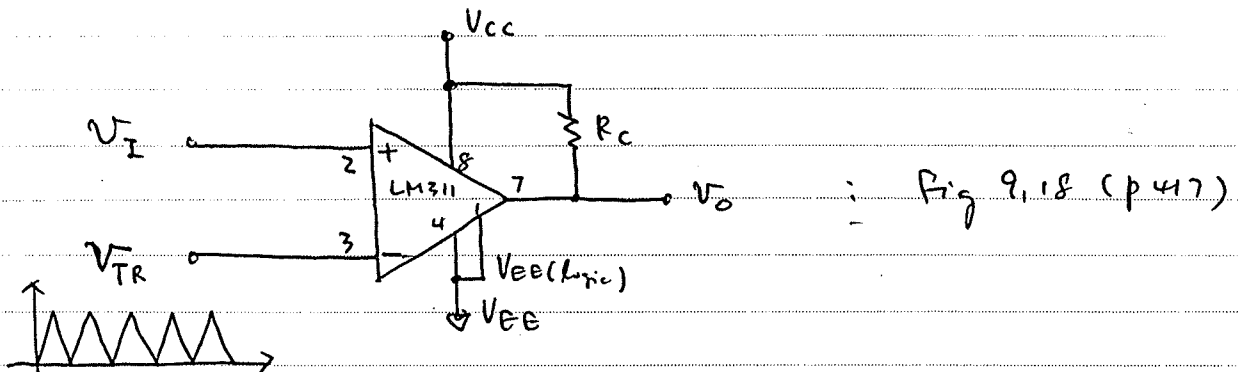


Fig 9.18 (p 417)

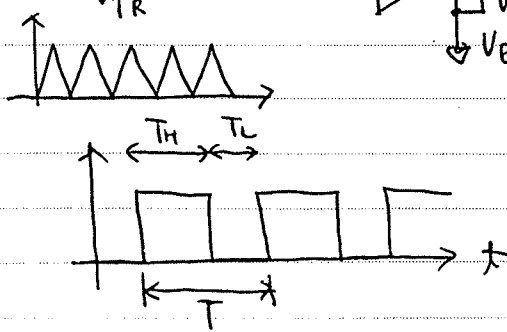


Duty cycle

$$D(\%) = \frac{T_H}{T_L + T_H} \times 100$$

### 9.3 Schmitt Triggers



- positive feedback

### \* Inverting Schmitt Trigger

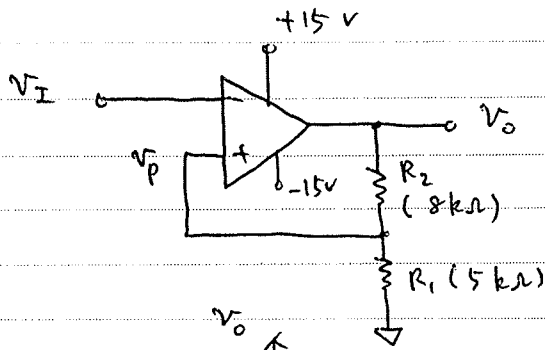

$$V_{TH} = \frac{R_1}{R_1 + R_2} V_{OH}$$

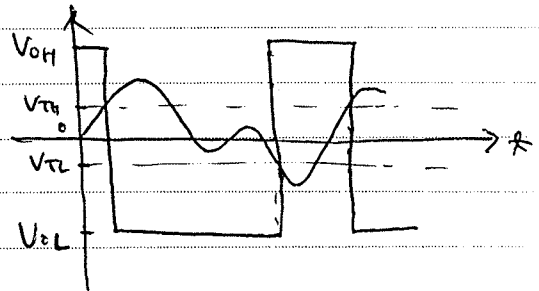
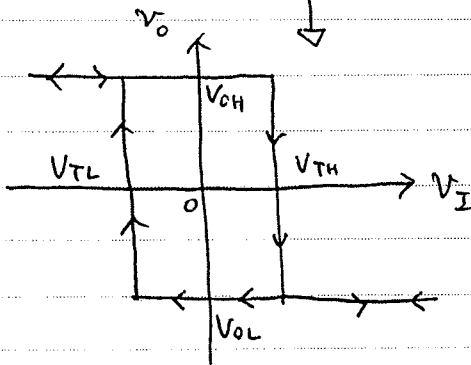
$$V_{TL} = \frac{R_1}{R_1 + R_2} V_{OL}$$



- hysteresis
- hysteresis width  $\Delta U_T = V_{TH} - V_{TL}$   

$$= \frac{R_1}{R_1 + R_2} (V_{OH} - V_{OL})$$

### \* Noninverting Schmitt Trigger

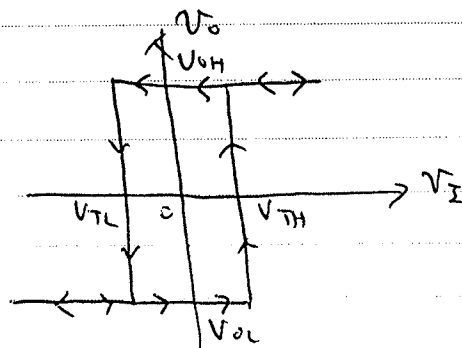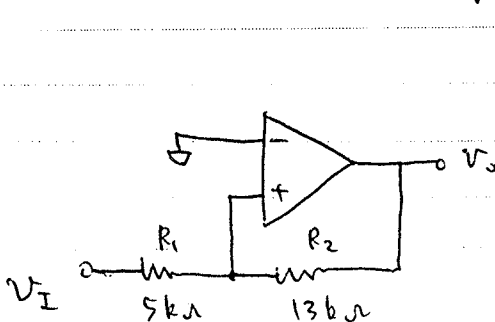


$$\left\{ \begin{aligned} V_{TH} &= -\frac{R_1}{R_2} V_{OL} \\ V_{TL} &= -\frac{R_1}{R_2} V_{OH} \\ \Delta V_T &= \frac{R_1}{R_2} (V_{OH} - V_{OL}) \end{aligned} \right.$$

- \* UTC offsetting on Single Supply Schmitt Trigger
  - Fig 9.22 (p 421)
  - Fig 9.23 (p 422)

- \* Hysteresis
  - Eliminate comparator chatter (Fig 9.24 & Fig 9.25 in p 423)

#### 9.4 Precision Rectifiers

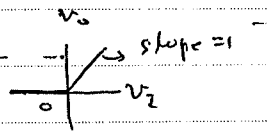


- HWR (half-wave rectifier)

$$v_o = \begin{cases} v_i & \text{for } v_i > 0 \\ 0 & \text{for } v_i \leq 0 \end{cases}$$



- FWR (full-wave rectifier)
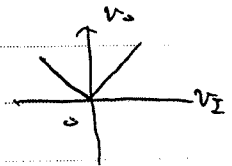
$$v_o = \begin{cases} v_i & \text{for } v_i > 0 \\ -v_i & \text{for } v_i \leq 0 \end{cases}$$




OR  $v_o = |v_i|$   
 $\Rightarrow$  absolute-value circuit


\* Diode

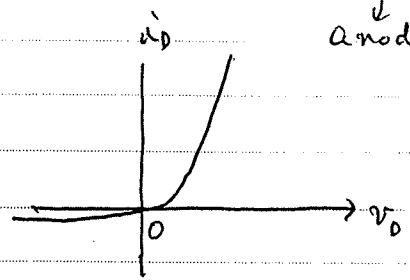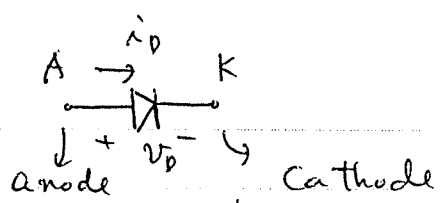

( $I_{SM} = 1$  diode)


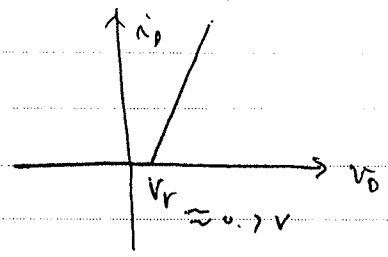


( $V_r = 0.7V$  model)

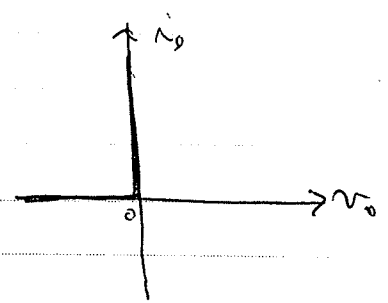


( $I_r = 10^{-6} A$  diode)

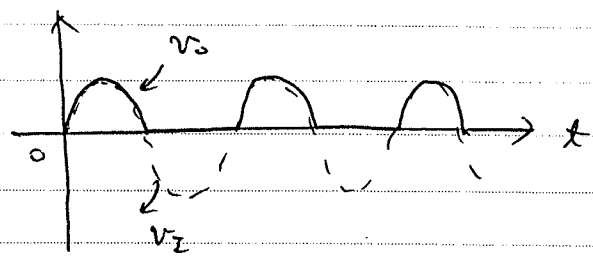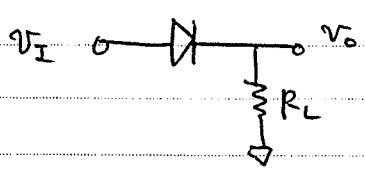$\begin{cases} v_D > V_r & : \text{forward bias, ON} \\ v_D < V_r & : \text{reverse bias, OFF} \end{cases}$



\* Half-Wave Rectifier

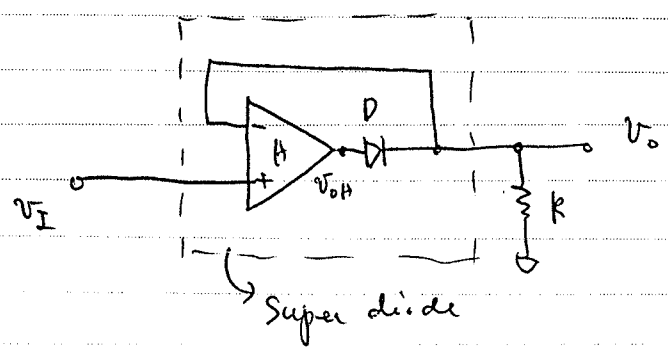


(i)  $V_I > 0 \rightarrow V_{OA} > 0 \rightarrow D \text{ ON (Fig 9.28a)}$   
 $\rightarrow v_o = v_I, \quad v_{OA} = v_o + V_r$

(!!)  $V_I < 0 \rightarrow V_{OA} < 0 \rightarrow D \text{ OFF (Fig 9.28b)}$   
 $\rightarrow v_o = 0, \quad v_{OA} = V_{OL}$




\* Improved HWR

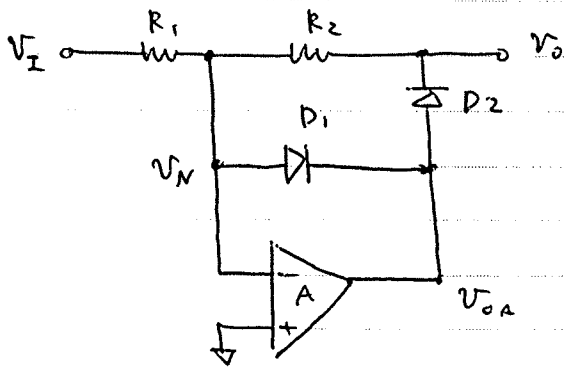


$-V_{OL} \text{ (on)}$

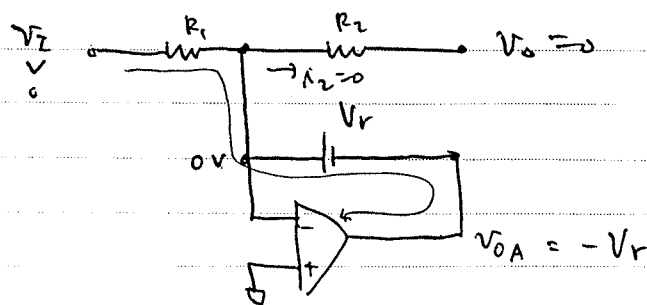
(i)  $V_I > 0 \rightarrow D1 \text{ ON} \rightarrow v_N = 0, \quad v_{OA} = -V_r$   
 $\rightarrow D2 \text{ OFF} \rightarrow v_o = 0$



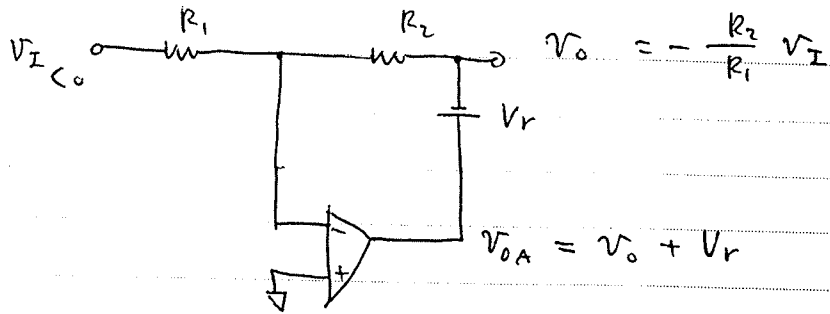
(!!)  $V_I < 0 \rightarrow v_{OA} > 0 \rightarrow D2 \text{ ON} \rightarrow v_N = 0, \quad D1 \text{ OFF}$   
 $\rightarrow \begin{cases} v_o = -\frac{R_2}{R_1} v_I \\ v_{OA} = v_o + V_r \end{cases}$


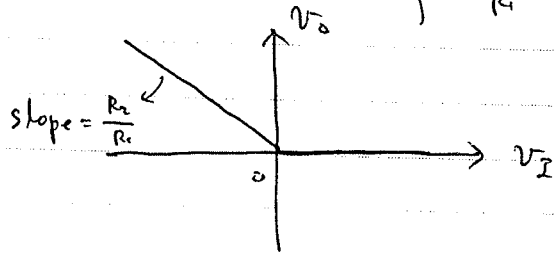
$$\Rightarrow v_o = \begin{cases} 0 & \text{for } v_I > 0 \\ -\frac{R_2}{R_1} v_I & \text{for } v_I < 0 \end{cases}$$




\* Full-Wave Rectifier

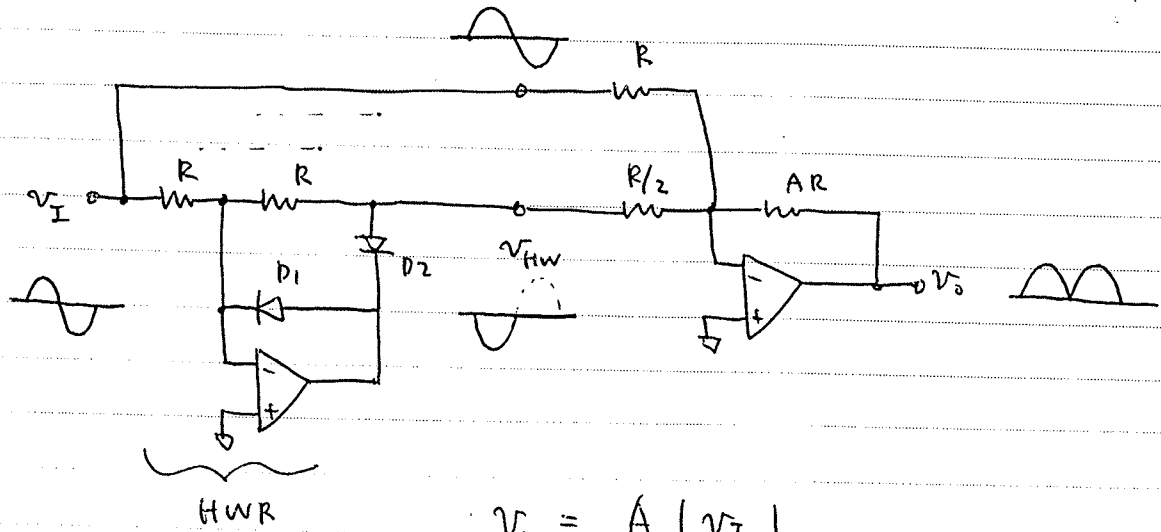

$$\begin{aligned} v_o &= A |v_I| \\ &= -A v_I - 2A v_{HW} \\ &= -A (v_I + 2 v_{HW}) \end{aligned}$$



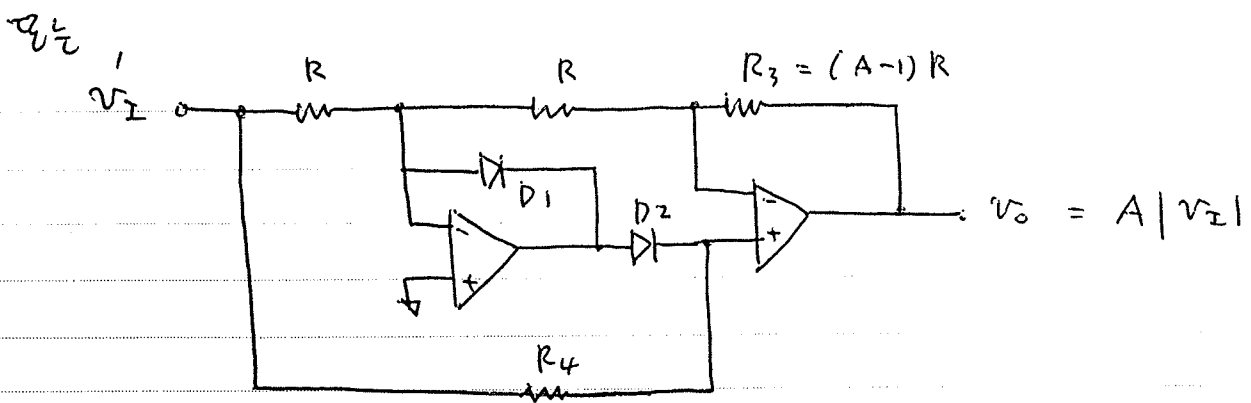

\* Ac - dc Converter

Handwritten notes in Hindi:  $\frac{2}{\pi}$  and  $\frac{1}{\sqrt{2}}$

$$V_{avg} = \frac{1}{T} \int_0^T |v(t)| dt$$


Handwritten note:  $\frac{2}{\pi}$  and  $\frac{1}{\sqrt{2}}$

$$v(t) = V_m \sin 2\pi ft \quad \text{or } |v(t)| \quad V_{avg} = \frac{2V_m}{\pi} = 0.637 V_m$$



$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$v(t) = V_m \sin 2\pi ft \quad \text{or } |v(t)| \quad V_{rms} = \frac{V_m}{\sqrt{2}} = 0.707 V_m$$

Fig 9.32 (p 430) : rms calibration.

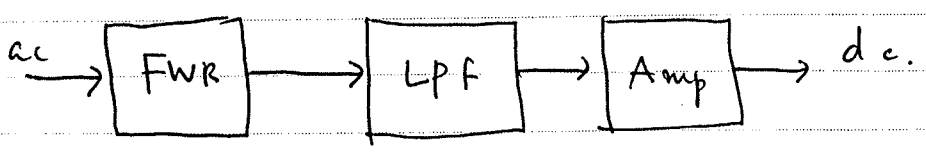


## 9.5 Analog Switch

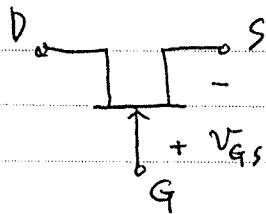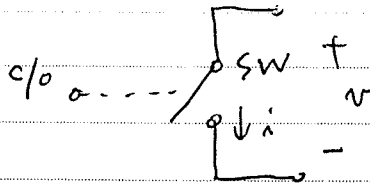

n-channel JFET

$$\begin{cases} V_{GS} = 0 \rightarrow \text{D-S ON} \\ V_{GS} < V_{GS(\text{off})} \rightarrow \text{D-S OFF} \end{cases}$$
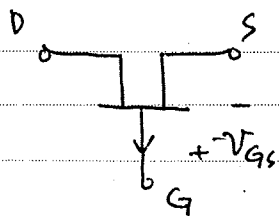
$$-4V \leq V_{GS(\text{off})} \leq -10V$$



p-channel JFET


$$\begin{cases} V_{GS} = 0 \rightarrow \text{D-S ON} \\ V_{GS} > V_{GS(\text{off})} \rightarrow \text{D-S OFF} \end{cases}$$

$$4V \leq V_{GS(\text{off})}$$


① MOSFET Switch

② CMOS (Max)

< 4051  
< 4052

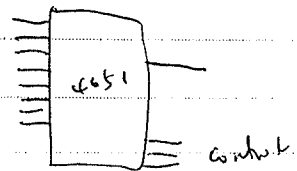

### 9.6 Peak Detector

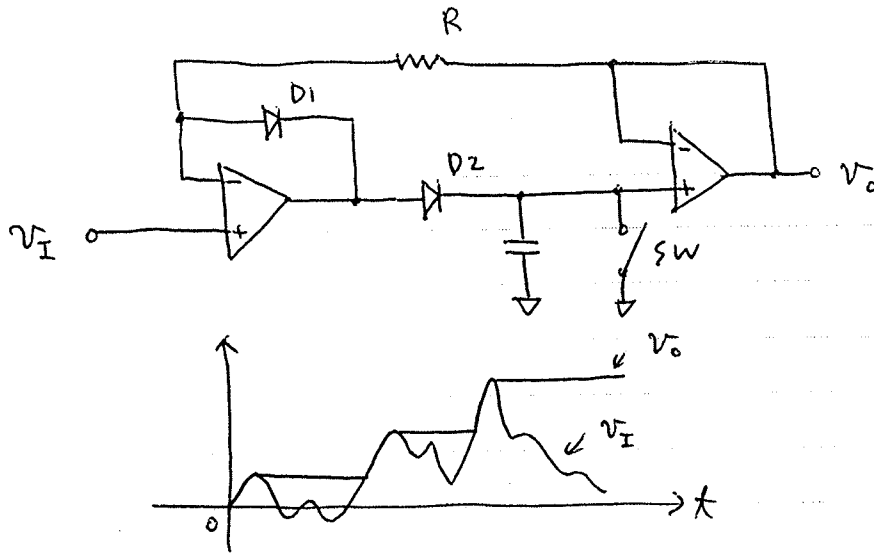

### 9.7 Sample - And - Hold Amplifier

Fig 9.44 and Fig 9.45 (p 400)