

Chapter 3 Active Filters : Part I

Filter :

Frequency Response $H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$

$$\left\{ \begin{array}{l} |H(j\omega)| : \text{magnitude response (gain)} \\ \angle H(j\omega) : \text{phase " (phase shift)} \end{array} \right.$$

* Common Frequency Responses

$$\left\{ \begin{array}{l} \text{Lowpass} \\ \text{Highpass} \\ \text{Bandpass} \\ \text{Band-reject (notch)} \\ \text{All-pass (delay filter)} \end{array} \right\} \Rightarrow \text{Fig 3.1}$$

$$\Rightarrow \left\{ \begin{array}{l} \text{cutoff frequency, } \omega_c = 2\pi f_c \\ \text{pass band (radio tuning circuitry)} \\ \text{stop band (notch filter)} \\ \text{transition band} \end{array} \right.$$

See Fig 3.2 (effect of filtering)

* Active filters : filters incorporating amplifiers.

cf) passive filters

* Discuss RC filter (LP & HP)

43

3.1 Transfer function

$$\frac{1}{sC} \Rightarrow Z_C = \frac{1}{sC} \quad : \text{ complex impedance}$$

$$sL \Rightarrow Z_L = sL \quad : \text{ complex impedance}$$

$$s = \sigma + j\omega \quad : \text{ complex frequency}$$

$$\left\{ \begin{array}{l} V = Z(s) I \quad : \text{ ohm's law} \\ \text{KVL} \\ \text{KCL} \\ \text{Voltage and current division} \\ \text{Superposition} \end{array} \right.$$

X_i : input, X_o : output

$$X_i(s) = \int_0^{\infty} f(t) e^{-st} dt \quad H(s) = \frac{X_o}{X_i} \quad : \text{ transfer function}$$

$$X_o(t) = \mathcal{L}^{-1} \left\{ H(s) X_i(s) \right\}$$

In linear circuits,

$$H(s) = \frac{N(s)}{D(s)} = \frac{a_m s^m + \dots + a_1 s + a_0}{b_n s^n + \dots + b_1 s + b_0}$$

↳ rational function of s
(#2/187)

m and n : degree

n : order of filter.

$$N(s) \Big|_{s=z_i} = 0 \Rightarrow s = z_i : \text{zero}$$

$$D(s) \Big|_{s=p_i} = 0 \Rightarrow s = p_i : \text{pole}$$

$$H(s) = H_0 \frac{(s-z_1)(s-z_2) \cdots (s-z_m)}{(s-p_1)(s-p_2) \cdots (s-p_m)}$$

$$H_0 = \frac{a_m}{b_n} : \text{scaling factor}$$

roots : critical frequency or
characteristic frequency

- real

- complex conjugate

* Example 3.1 \Rightarrow M_{2000} (Fig. 3.3)

* $H(s)$ and Stability

BIBO \Rightarrow stable

CASE I $H(s)$ has a real pole.
 $\mathcal{L}^{-1} \left\{ \frac{A_k}{s - \sigma_k} \right\} = A_k e^{\sigma_k t} u(t)$

$\sigma_k < 0$: decay

$\sigma_k = 0$: constant

$\sigma_k > 0$: divergence

CASE II. $H(s)$ has a complex conjugate poles

$$\mathcal{L}^{-1} \left\{ \frac{A_k}{s - (\sigma_k + j\omega_k)} + \frac{A_k^*}{s - (\sigma_k - j\omega_k)} \right\}$$

$$= 2 |A_k| e^{\sigma_k t} \cos(\omega_k t + \angle A_k)$$

We need $\sigma_k < 0$ for stability.

" A circuit is stable if all poles lie in the left half of the s plane (LHP) "

* $H(s)$ and Frequency Response

Stable circuit (all poles in LHP)
 \Downarrow
 transient response die out

\Rightarrow We will study "steady-state response" only.

$$x_i(t) = X_{im} \cos(\omega t + \theta_i)$$

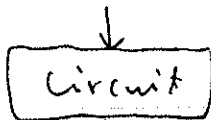


Fig. 3.4

↓

$$x_o(t) = X_{om} \cos(\omega t + \theta_o)$$


$$s = \sigma + j\omega$$

$$\begin{cases} \sigma \Rightarrow \text{transient response} \\ \omega \Rightarrow \text{steady state response} \end{cases}$$

\Rightarrow We will compute $H(s)$ on $j\omega$ -axis only to find out steady state response.

Let $s \rightarrow j\omega = j2\pi f$, then

$$\begin{cases} X_{om} = |H(j\omega)| X_{im} \\ \theta_o = \angle H(j\omega) + \theta_i \end{cases}$$

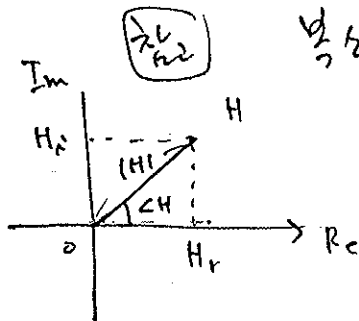

$$\frac{H_i}{H_r} = \tan^{-1} \frac{H_i}{H_r}$$

$$H = H_r + jH_i = |H| \angle \angle H$$

$$\begin{cases} |H| : \text{magnitude or modulus} \\ \angle H : \text{argument or phase angle} \\ H_r : \text{real part} \\ H_i : \text{imaginary part} \end{cases}$$

$$|H| = \sqrt{H_r^2 + H_i^2}$$

$$\angle H = \tan^{-1} \frac{H_i}{H_r} \quad \text{if } H_r > 0$$

$$\angle H = 180^\circ - \tan^{-1} \frac{H_i}{H_r} \quad \text{if } H_r < 0$$

$$\begin{aligned} |H_1 H_2| &= |H_1| |H_2| \\ \angle (H_1 H_2) &= \angle H_1 + \angle H_2 \end{aligned}$$


$$\begin{aligned} |H_1/H_2| &= |H_1|/|H_2| \\ \angle(H_1/H_2) &= \angle H_1 - \angle H_2 \end{aligned}$$

Cases.

- ① Circuit \rightarrow plot $|H(j\omega)|$ & $\angle H(j\omega)$ (Bode plots)
 ② $H(j\omega) \rightarrow$ find $H(s)$ & pole-zero plot
 ③ $H(j\omega) \rightarrow$ design a circuit
 ④ Circuit \rightarrow find $H(j\omega)$ experimentally

* Bode plots

$$20 \log_{10} |H| = |H|_{dB}$$

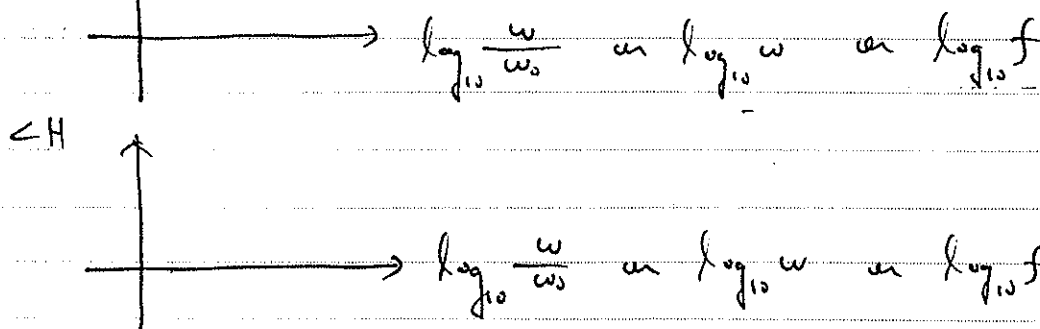


$$\begin{aligned} |H_1 H_2|_{dB} &= |H_1|_{dB} + |H_2|_{dB} \\ |H_1/H_2|_{dB} &= |H_1|_{dB} - |H_2|_{dB} \\ |1/H_1|_{dB} &= -|H_1|_{dB} \end{aligned}$$

⊙ Asymptotic approximation

$$\begin{cases} H \approx H_r & \text{if } |H_r| \gg |H_i| \\ H \approx j H_i & \text{if } |H_i| \gg |H_r| \end{cases}$$

3.2 First-Order Active Filter

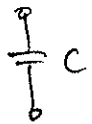


$$Z_c = \frac{1}{sC} = \frac{1}{j\omega C}$$

$\lim_{\omega \rightarrow 0} Z_c = \infty$: for DC, cap. is open

$\lim_{\omega \rightarrow \infty} Z_c = 0$: for very high freq., cap. is short

* Differentiator

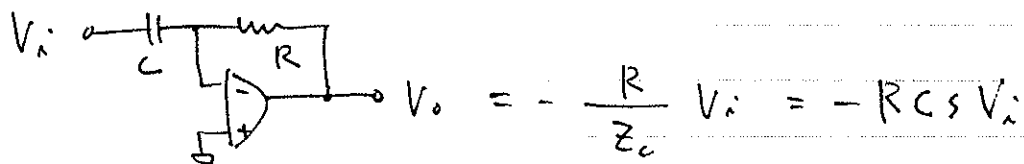


$H(s) = -RCs$: a zero at the origin

$$H(j\omega) = -j\omega RC$$

Let $\omega_0 = \frac{1}{RC}$ (scaling freq.),
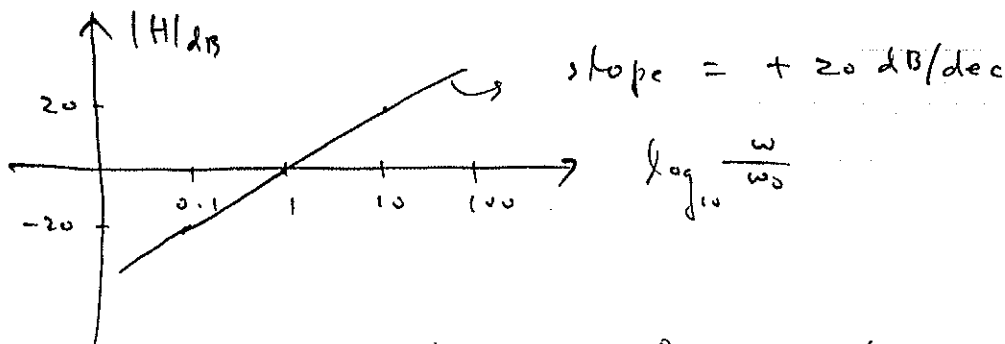
$$H(j\omega) = -\frac{j\omega}{\omega_0} = \frac{\omega}{\omega_0} \angle -90^\circ$$




$\angle H(j\omega) = -90^\circ \Rightarrow 90^\circ$ phase lag

at $\omega = \omega_0$, $|Z_c| = R$ and $|H|_{dB} = 0$

$\Rightarrow \omega_0$ is the unity-gain frequency

* Integrator

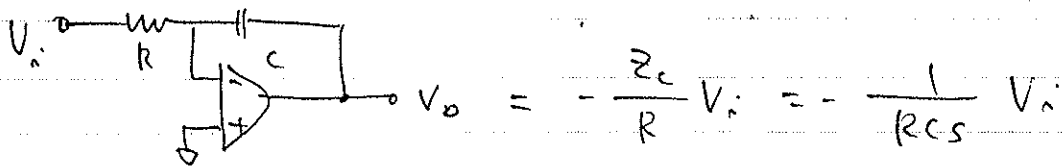


(Miller integrator or inverting integrator)


$$H(s) = -\frac{1}{RCs} \quad ; \quad \text{a pole at the origin}$$

$$H(j\omega) = -\frac{1}{j\omega/\omega_0} = \frac{1}{\omega/\omega_0} \angle +90^\circ$$
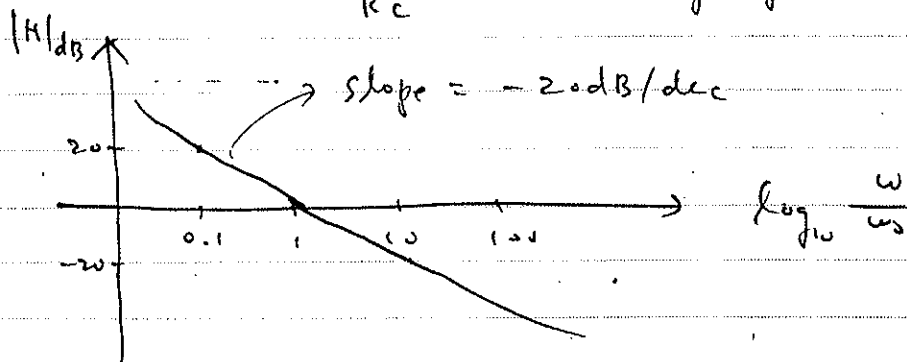
$$\omega_0 = \frac{1}{RC} \quad ; \quad \text{unity-gain freq.}$$


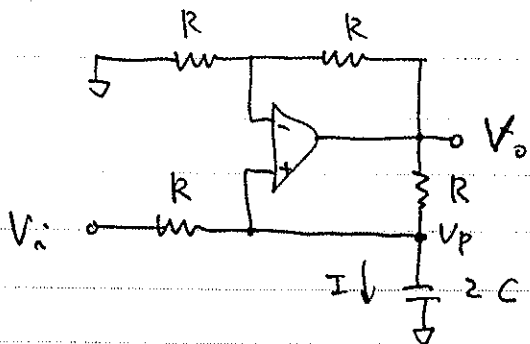
$$\angle H = +90^\circ \Rightarrow 90^\circ \text{ phase lead}$$



: Deboo integrator


$$I = \frac{V_i}{R} \quad (\because \text{Howland current pump})$$

$$V_p = \frac{I}{2sC} = \frac{V_i}{2sRC}$$

$$V_o = \left(1 + \frac{R}{R}\right) V_p = \frac{V_i}{sRC}$$

$$H(s) = \frac{1}{sRC}$$
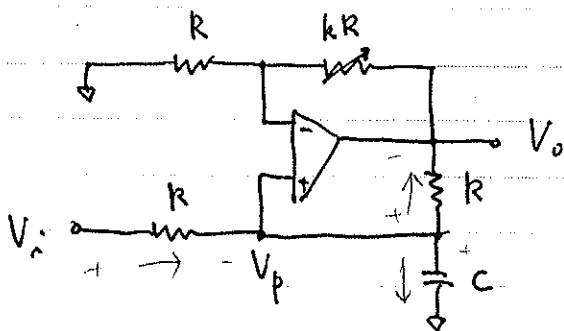
$$\angle H = -90^\circ \Rightarrow 90^\circ \text{ phase lag.}$$



$$\left(\begin{array}{l} \text{NIC} \Rightarrow -\frac{R}{kR} R = -\frac{R}{k}, \quad k \geq 0 \\ \text{Net resistance seen by } C = R \parallel \left(-\frac{R}{k}\right) \\ = \frac{R}{1-k} \end{array} \right)$$


$$\left\{ \begin{aligned} \frac{V_i - V_p}{R} &= sC V_p + \frac{V_p - V_o}{R} \\ V_o &= (1 + kR/R) V_p = (1+k) V_p \end{aligned} \right.$$

$$\Rightarrow V_o = \frac{1+k}{sRC + 1-k} V_i$$


$$\therefore H(s) = \frac{1+k}{sRC + 1-k}$$

$$p = -\frac{1-k}{RC}$$

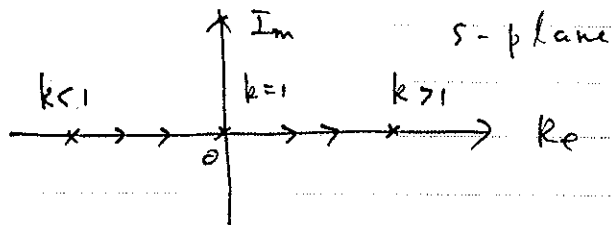natural response, $V_o(t) = V_o(0) e^{-t(1-k)/RC} u(t)$



* Low-pass Filter with Gain

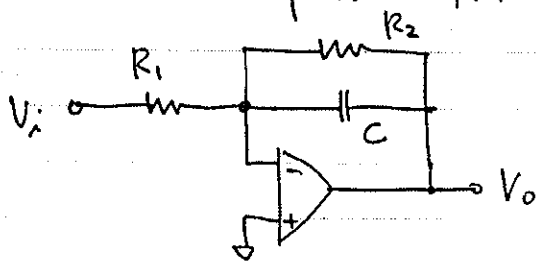


$$\begin{aligned} Z_2 &= R_2 \parallel \frac{1}{sC} \\ &= \frac{R_2 \cdot \frac{1}{sC}}{R_2 + \frac{1}{sC}} \\ &= \frac{R_2}{1 + sR_2C} \end{aligned}$$

$$H(s) = -\frac{Z_2}{R_1} = -\frac{R_2}{R_1} \frac{1}{1 + sR_2C}$$

$$p = -\frac{1}{R_2 C}$$

$$H(j\omega) = H_0 \frac{1}{1 + j\omega/\omega_0}$$

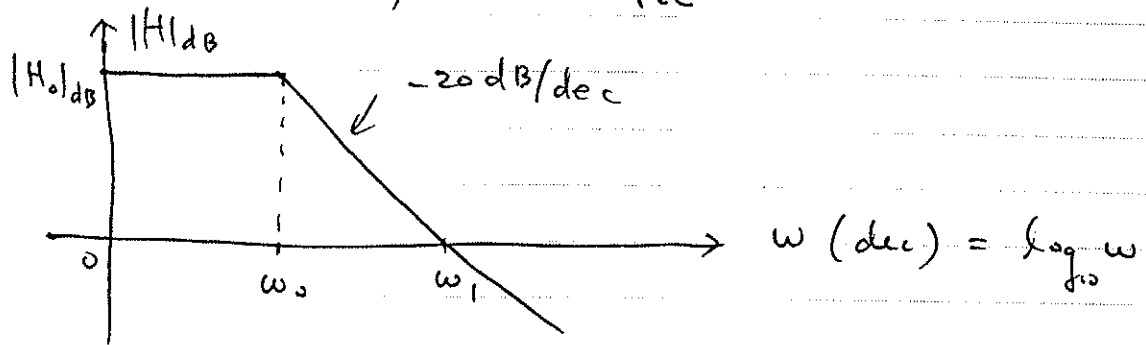dc gain $\leftarrow H_0 = -\frac{R_2}{R_1}, \quad \omega_0 = \frac{1}{R_2 C}$



at $\omega = \omega_0$, $|H| = |H_0| / |1 + j| = \frac{1}{\sqrt{2}} |H_0|$

OR, $|H|_{dB} = |H_0|_{dB} - 3 \text{ dB}$


$\Rightarrow \omega_0$: -3 dB cutoff frequency

$0 \sim \omega_0$: 3 dB bandwidth of LPF

$\therefore \omega > \omega_0 \Rightarrow$ (lossy) integrator

Example 3.4

* High-pass Filter with Gain

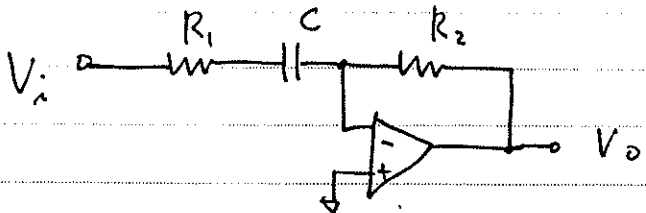

$$Z_1 = R_1 + \frac{1}{sC}$$

$$= \frac{1 + sR_1C}{sC}$$


$$H(s) = -\frac{R_2}{Z_1} = -\frac{R_2 sC}{1 + sR_1C} = -\frac{R_2}{R_1} \frac{sR_1C}{1 + sR_1C}$$

$$z = 0, \quad p = -\frac{1}{R_1C}$$


$$H(j\omega) = H_0 \frac{j\omega/\omega_0}{1 + j\omega/\omega_0}$$

high-freq.
gain
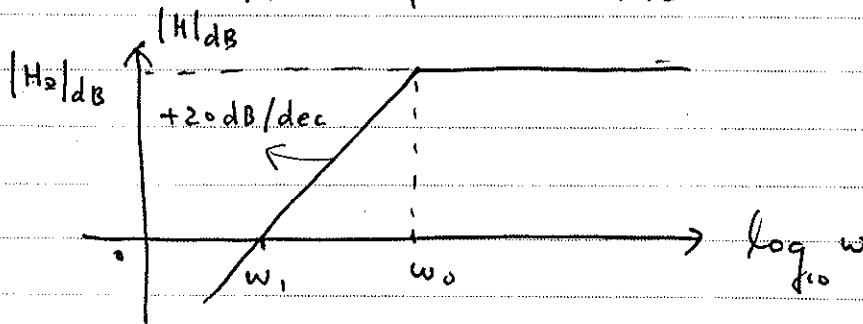
$$H_0 = -\frac{R_2}{R_1}, \quad \omega_0 = \frac{1}{R_1C} \quad \therefore -3\text{dB cutoff freq.}$$



* Wideband Band-pass Filter

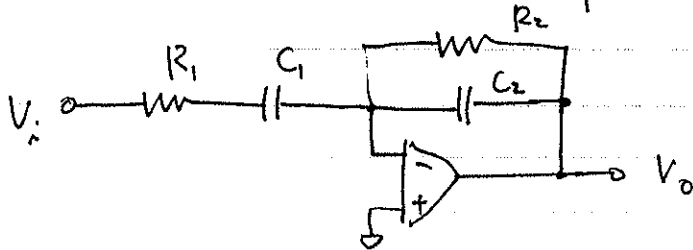

$$Z_1 = R_1 + \frac{1}{sC_1} = \frac{1 + sR_1C_1}{sC_1}$$


$$Z_2 = R_2 \parallel \frac{1}{sC_2} = \frac{R_2}{1 + sR_2C_2}$$

$$H(s) = \frac{Z_2}{Z_1} = \frac{R_2}{R_1} \cdot \frac{R_1C_1s}{1 + R_1C_1s} \cdot \frac{1}{1 + R_2C_2s}$$

$$z = 0, \quad p = -\frac{1}{R_1C_1} \quad \& \quad -\frac{1}{R_2C_2}$$


$$H(j\omega) = H_0 \frac{j\omega/\omega_L}{(1 + j\omega/\omega_L)(1 + j\omega/\omega_H)}, \quad \omega_H > \omega_L$$

- $H_0 = -\frac{R_2}{R_1}$: midfrequency gain (passband gain)
- ω_L : low -3dB cutoff freq.
- ω_H : high -3dB " "

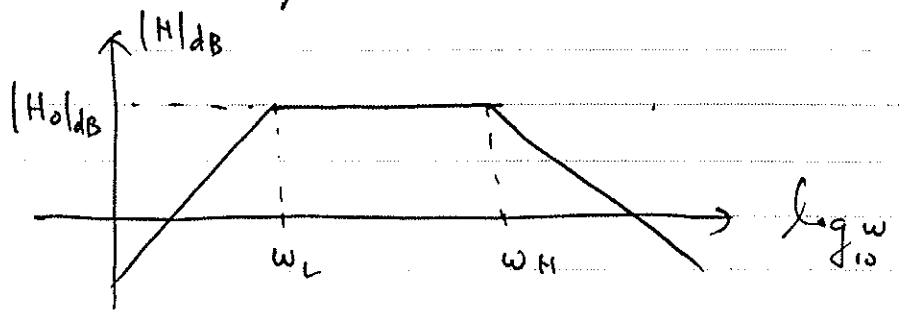

Example 3.5

* Phase Shifter

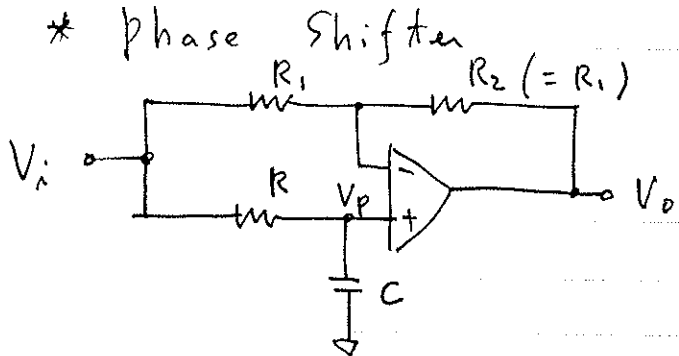

$$V_p = \frac{\frac{1}{sC}}{R + \frac{1}{sC}} V_i = \frac{1}{1 + RCs} V_i$$


$$V_o = -\frac{R_2}{R_1} V_i + \left(1 + \frac{R_2}{R_1}\right) V_p = -V_i + 2V_p \quad (R_2 = R_1 = R)$$

$$= -V_i + \frac{2}{1 + RCs} V_i$$

$$= \frac{1 - RCs}{1 + RCs} V_i$$

$$H(s) = \frac{1 - RCs}{1 + RCs} \Rightarrow z = \frac{1}{RC}, \quad p = -\frac{1}{RC}$$
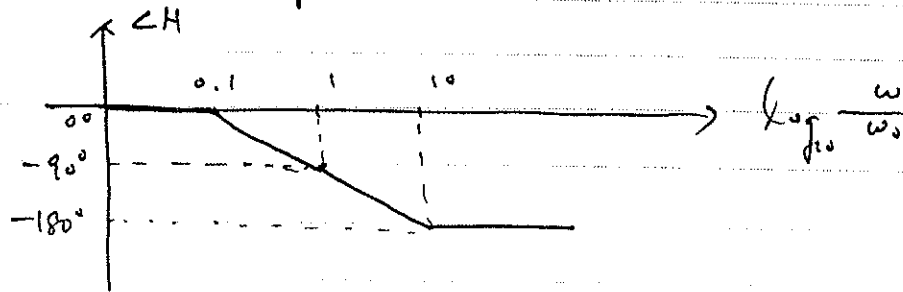
$$H(j\omega) = \frac{1 - j\omega/\omega_0}{1 + j\omega/\omega_0} = 1 \angle -2 \tan^{-1} \frac{\omega}{\omega_0}$$



phase shift \propto freq. \Rightarrow "same time delay"

$$\sin(\omega t + \alpha t) \Rightarrow \sin\left(\omega t + \underbrace{\alpha t}_{\tau \omega}\right)$$

$$\frac{1}{1+j\omega/\omega_0} \quad \text{LPF}, \quad \frac{j\omega/\omega_0}{1+j\omega/\omega_0} \quad \text{HPF}, \quad \frac{1-j\omega/\omega_0}{1+j\omega/\omega_0} \quad \text{All pass} : \text{First order filter}$$

56

3.3 Audio Filter Applications

Fig 3.13

Fig 3.14

Fig 3.15

Fig 3.16

3.4 Standard Second-Order Responses

이차 필터의
H(s)가

$$H(s) = \frac{N(s)}{(s/\omega_0)^2 + 2\zeta(s/\omega_0) + 1}$$

$$\begin{cases} N(s) : \text{polynomial } (m \leq 2) \\ \omega_0 : \text{undamped natural freq.} \\ \zeta : \text{damping ratio } (\text{zeta}) \end{cases}$$

$$p_{1,2} = (-\zeta \pm \sqrt{\zeta^2 - 1}) \omega_0$$


① $\zeta > 1$: over damped
 $\begin{cases} \text{real \& negative poles} \\ \text{natural response} = \text{two decaying exponentials} \end{cases}$

② $0 < \zeta < 1$: under damped
 $\begin{cases} \text{complex conjugate poles} : -\zeta\omega_0 \pm j\omega_0\sqrt{1-\zeta^2} \\ \text{natural response} = \text{damped sinusoids} \end{cases}$

$$x(t) = 2|A| e^{-\zeta\omega_0 t} \cos(\omega_0\sqrt{1-\zeta^2} t + \angle A)$$

② $\zeta = 0$: undamped
 { imaginary poles : $\pm j\omega_0$
 { natural response : sinusoids with ω_0

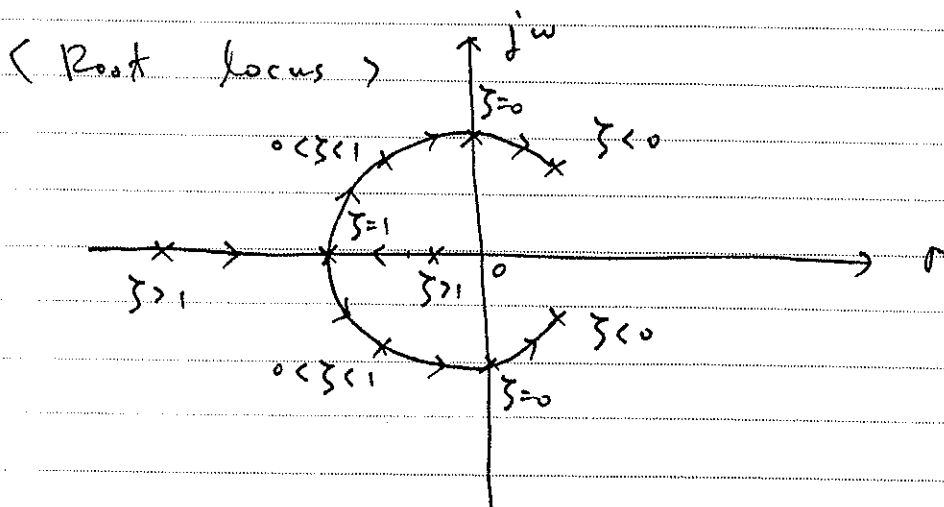④ $\zeta < 0$: diverging
 poles in RHP \Rightarrow unstable



$$H(j\omega) = \frac{N(j\omega)}{1 - (\omega/\omega_0)^2 + (j\omega/\omega_0)/\theta}$$

$$\theta = \frac{1}{2\zeta}$$

* Low pass Response, H_{lp}

$$H(j\omega) = H_{lp} H_{lp}(j\omega) = H_{lp} \frac{1}{1 - (\omega/\omega_0)^2 + (j\omega/\omega_0)/\theta}$$

H_{lp} : dc gain

① $w/w_0 \ll 1$, $H_{cp} \rightarrow 1$ $\therefore |H_{cp}|_{dB} = 0$

② $w/w_0 \gg 1$, $H_{cp} \rightarrow -1/(w/w_0)^2$
 $\therefore |H_{cp}|_{dB} = 20 \log_{10} \left[\frac{1}{(w/w_0)^2} \right]$
 $= -40 \log_{10} (w/w_0)$

③ $w/w_0 = 1$, $H_{cp} = -jQ$ $\therefore |H_{cp}|_{dB} = Q_{dB}$

$Q = 0.5 \sim 100$

$Q > 1 \Rightarrow$ peaking at $w = w_0$

Fig 3.19(a)

(i) Butterworth response : $\left\{ \begin{array}{l} Q = \frac{1}{\sqrt{2}} = 0.707 \\ \text{maximally flat} \\ |H_{cp}|_{dB} = -3 \text{ dB} \end{array} \right.$
 at $w = w_0$
 \Downarrow
 $w_0 = -3 \text{ dB cut-off freq.}$

(ii) $Q > \frac{1}{\sqrt{2}}$: Peaked response
 $|H_{cp}|_{max} = \frac{Q}{\sqrt{1 - \frac{1}{4}Q^2}}$
 at $w/w_0 = \sqrt{1 - \frac{1}{4}Q^2}$

(iii) $Q > 5$, $w/w_0 \approx 1$, $|H_{cp}|_{max} \approx Q$

(iv) $Q < 1/\sqrt{2}$, $|H_{cp}|_{max} = 1$ at $w = 0$ (dc)

* High-pass Response, H_{HP}

$$H(j\omega) = \underbrace{H_{0HP}}_{\substack{\text{high-freq.} \\ \text{gain}}} H_{HP}(j\omega) = H_{0HP} \frac{-(\omega/\omega_0)^2}{1 - (\omega/\omega_0)^2 + (j\omega/\omega_0)/Q}$$

Fig 3.19 (b)

H_{HP} mim $j\omega/\omega_0 \approx 1/(j\omega/\omega_0) \approx \omega^{-1} \rightarrow H_{HP}$
 $|H_{HP}| \approx \omega^{-2}$ mirror image.

* Band-pass Response, H_{BP}

$$H(j\omega) = \underbrace{H_{0BP}}_{\substack{\text{resonance gain or passband gain} \\ \text{or midband gain}}} H_{BP}(j\omega) = H_{0BP} \frac{(j\omega/\omega_0)/Q}{1 - (\omega/\omega_0)^2 + (j\omega/\omega_0)/Q}$$

$$\textcircled{1} \omega/\omega_0 \ll 1, \quad H_{BP} \rightarrow (j\omega/\omega_0)/Q$$

$$\begin{aligned} \therefore |H_{BP}|_{dB} &= 20 \log_{10} [(\omega/\omega_0) / Q] \\ &= 20 \log_{10} (\omega/\omega_0) - Q_{dB} \end{aligned}$$

$$\textcircled{2} \omega/\omega_0 \gg 1, \quad H_{BP} \rightarrow -j / (\omega/\omega_0) Q$$

$$\therefore |H_{BP}|_{dB} = -20 \log_{10} (\omega/\omega_0) - Q_{dB}$$

③ $\omega/\omega_0 = 1$, $H_{Bp} = 1$ $\therefore |H_{Bp}|_{dB} = 0$


$|H_{Bp}|$ is maximum at $\omega = \omega_0$
 peak freq. or resonance freq.

$\left\{ \begin{array}{l} \omega > \omega_0 \text{ or } \omega < \omega_0 \text{ } \pm 20 \text{ dB/dec} \\ \omega > \omega_0 \text{ or } \omega < \omega_0 \text{ } \text{slope } \rightarrow \pm \end{array} \right.$

Fig 3.20

$BW = \omega_H - \omega_L$

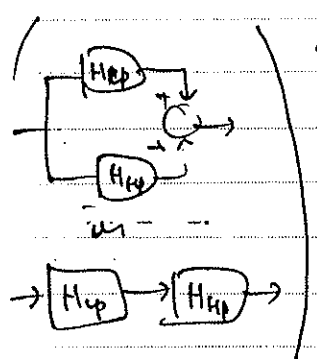$\left\{ \begin{array}{l} \omega_L = \omega_0 \left(\sqrt{1 + \frac{1}{4}Q^2} - \frac{1}{2}Q \right) \text{ : } -3\text{dB cutoff freq.} \\ \omega_H = \omega_0 \left(\sqrt{1 + \frac{1}{4}Q^2} + \frac{1}{2}Q \right) \text{ : } \text{ " } \end{array} \right.$



$\Rightarrow Q = \frac{\omega_0}{BW}$: selectivity -

* Notch Response, H_N

$H(j\omega) = H_{HP} H_N(j\omega)$
 \hookrightarrow dc or high-freq. gain



$H_N(j\omega) = \frac{1 - (\omega/\omega_0)^2}{1 - (\omega/\omega_0)^2 + (j\omega/\omega_0)/Q}$

$\left\{ \begin{array}{l} \text{pole pair : } \pm j\omega_0 \rightarrow \text{notch freq.} \\ \text{zeros : } \end{array} \right.$

Fig 3.21

$$\left\{ \begin{array}{l} \lim_{\omega \rightarrow 0} H_N \rightarrow 1 \quad \& \quad \lim_{\omega \rightarrow \infty} H_N \Rightarrow 1 \\ \lim_{\omega \rightarrow \omega_0} H_N \rightarrow 0 \\ \theta \uparrow \Rightarrow \text{narrower notch} \\ \omega_0 = \text{notch freq.} \end{array} \right.$$

$$H_N = H_{Hp} + H_{Hp} = 1 - H_{Bp}$$

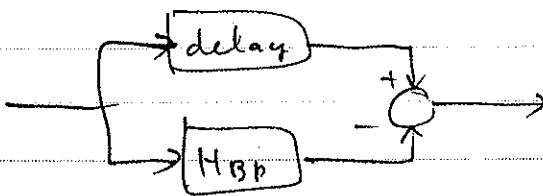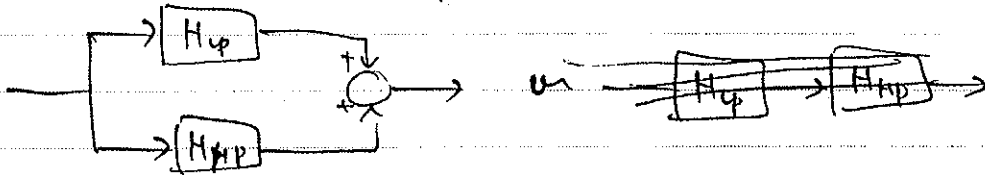

* All-pass Response ; H_{Ap}

$$H_{Ap}(j\omega) = \underbrace{H_{0Ap}}_{\text{gain}} H_{Ap}(j\omega)$$

$$H_{Ap}(j\omega) = \frac{1 - (\omega/\omega_0)^2 - (j\omega/\omega_0)/\theta}{1 - (\omega/\omega_0)^2 + (j\omega/\omega_0)/\theta}$$

$$\theta > 0.5$$

↓

$$N(j\omega) = D^*(j\omega) \quad \text{with complex and symmetric poles and zeros}$$

↓

$$|H_{Ap}| = 1$$

b2

$$\angle H_{Ap} = -2 \tan^{-1} \frac{(w/w_0)/Q}{1 - (w/w_0)^2}, \quad w/w_0 < 1$$

$$= -360^\circ - 2 \tan^{-1} \frac{(w/w_0)/Q}{1 - (w/w_0)^2}, \quad w/w_0 > 1$$

⇒ Fig 3.21.

$$H_{Ap} = H_{cp} - H_{Bp} + H_{Hp} = 1 - 2H_{Bp}$$

* Filter Measurements.

LPF

$$H_{cp}(j\omega) = H_{ocp}, \quad H_{cp}(j\omega_0) = -j H_{ocp} Q$$

at $\omega = \omega_0$, we have 90° phase shift

$$Q = |H_{cp}(j\omega_0)| / |H_{ocp}|$$

BPF

$$H_{Bp}(j\omega_0) = H_{oBp}$$



$$\angle H_{Bp}(j\omega_L) = \angle H_{oBp} - 45^\circ$$

$$\angle H_{Bp}(j\omega_H) = \angle H_{oBp} - 135^\circ$$


at $\omega = \omega_0$, 0° or 180° phase shift

$$Q = \frac{\omega_0}{\omega_H - \omega_L}$$

3.5 KRC Filters : $\rho < 10$

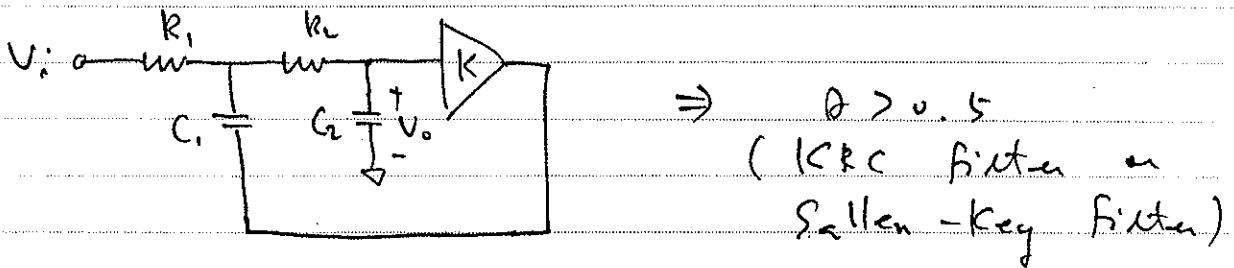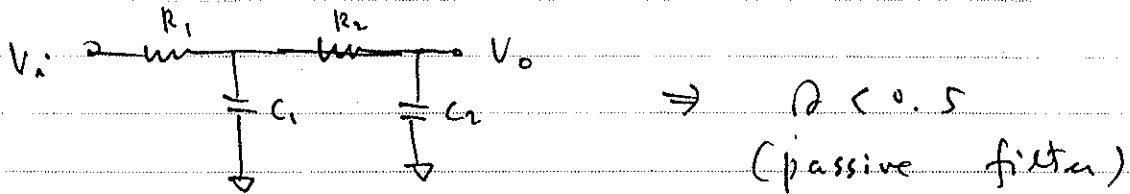

* Lowpass KRC Filter

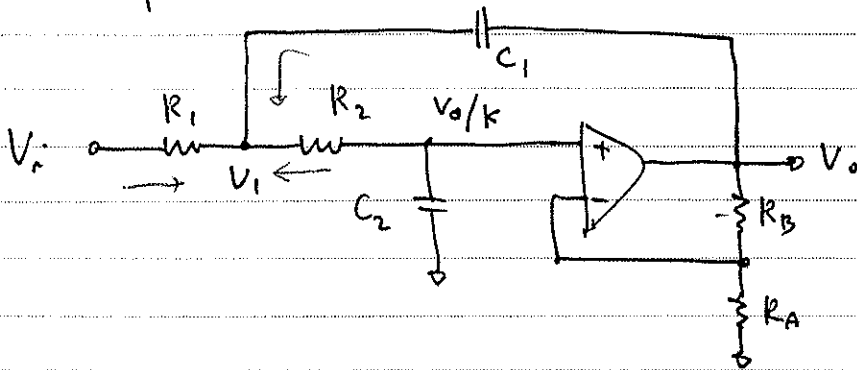

$$K = 1 + \frac{R_B}{R_A}$$

$$V_o = K \frac{1}{1 + sR_2C_2} V_1$$

$$\frac{V_i - V_1}{R_1} + \frac{V_o/K - V_1}{R_2} + \frac{V_o - V_1}{1/sC_1} = 0$$

$$\Rightarrow H(s) = \frac{V_o}{V_i} = \frac{K}{R_1 C_1 R_2 C_2 s^2 + [(1-K)R_1 C_1 + R_1 C_2 + R_2 C_2] s + 1}$$

$$H(j\omega) = K \frac{1}{1 - \omega^2 R_1 C_1 R_2 C_2 + j\omega [(1-K)R_1 C_1 + R_1 C_2 + R_2 C_2]}$$

$$H(j\omega) = H_{OLP} H_{FP}(j\omega) \text{ where}$$

$$H_{OLP} = K$$

$$\omega_0 = \frac{1}{\sqrt{R_1 C_1 R_2 C_2}}$$

$$\left(\because \left(\frac{\omega}{\omega_0} \right)^2 = \omega^2 R_1 C_1 R_2 C_2 \right)$$

$$\theta = \frac{1}{(1-K) \sqrt{R_1 C_1 / R_2 C_2} + \sqrt{R_1 C_2 / R_2 C_1} + \sqrt{R_2 C_2 / R_1 C_1}}$$

Designing

- ① R_1 design $\Rightarrow \omega_0$ design
- ② R_B design $\Rightarrow \theta$ design
- ③ K, R_1, C_1, R_2, C_2 design
 - equal component design
 - unity-gain design

* Equal-component KRC circuit ($\theta < 180^\circ$)

$$R_1 = R_2 = R, \quad C_1 = C_2 = C$$

$$H_{OLP} = K, \quad \omega_0 = \frac{1}{RC}, \quad \theta = \frac{1}{3-K}$$

$$\Rightarrow RC = \frac{1}{\omega_0}, \quad K = 3 - \frac{1}{\theta}, \quad R_B = (K-1)R_A$$

Example 3.8

Designing
 Equal-component
 unity-gain design
 Example 3.8

* Unity-Gain KRC circuit

$k = 1$

$R_2 = R, C_2 = C, R_1 = mR, C_1 = nC$

$H_{0HP} = 1, \omega_0 = \frac{1}{\sqrt{mn}RC}, \theta = \frac{\sqrt{mn}}{m+1}$

For a given n , $m=1$ maximizes θ .
 ($n = 4\theta^2$)

Design Procedure

① Choose C_1 & C_2 s.t.

$n \geq 4\theta^2$


② $m = k + \sqrt{k^2 - 1}$

where $k = \frac{n}{2\theta^2} - 1$

② Example 3.10

* High-pass KRC filter

⇒ LPF n/m R & C = 1 ; 1/3, 1/2, 1/3

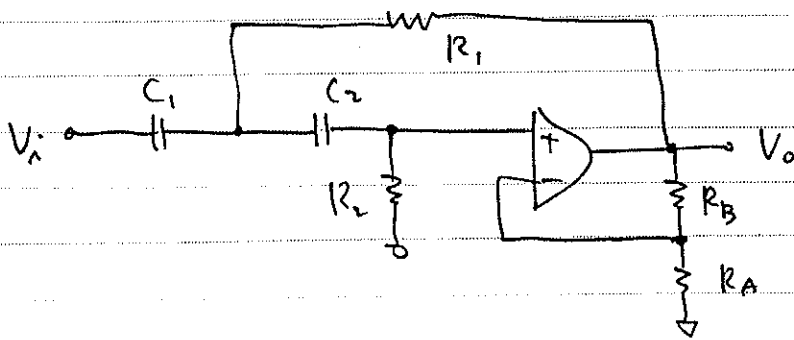


$H_{0HP} = k, \omega_0 = \frac{1}{\sqrt{R_1 C_1 R_2 C_2}}$

$\theta = \frac{1}{(1-k)\sqrt{R_2 C_2 / R_1 C_1} + \sqrt{R_1 C_2 / R_2 C_1} + \sqrt{R_1 C_1 / R_2 C_2}}$

③ Example 3.12

* Bandpass KRC filter

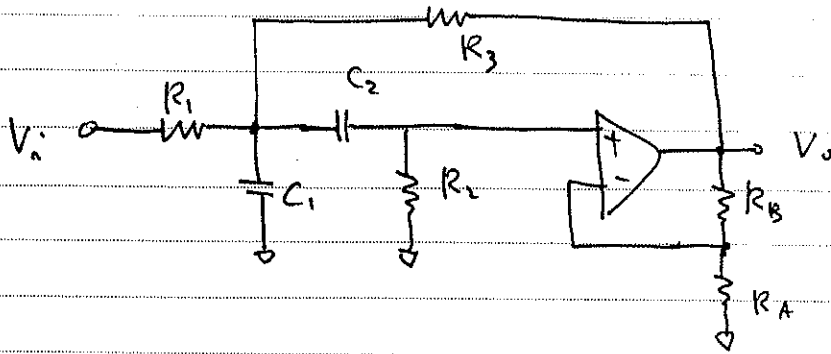

$$H_{oBP} = \frac{K}{1 + (1-K)R_1/R_3 + (1 + C_1/C_2)R_1/R_2}$$

$$\omega_0 = \frac{\sqrt{1 + R_1/R_3}}{\sqrt{R_1 C_1 R_2 C_2}}$$

$$Q = \frac{\sqrt{1 + R_1/R_3}}{[1 + (1-K)R_1/R_3] \sqrt{R_2 C_2 / R_1 C_1} + \sqrt{R_1 C_2 / R_2 C_1} + \sqrt{R_1 C_1 / R_2 C_2}}$$

Adjust K & Q

① Adjust $R_1 \Rightarrow \omega_0 \uparrow \downarrow$

② Adjust $R_B \Rightarrow Q \uparrow \downarrow$

③ $Q > \sqrt{2}/3 \Rightarrow \text{not possible}$


$$\begin{cases} R_1 = R_2 = R_3 = R \\ C_1 = C_2 = C \end{cases}$$

$$\Rightarrow H_{oBP} = \frac{K}{4-K}, \quad \omega_0 = \frac{\sqrt{2}}{RC}, \quad Q = \frac{\sqrt{2}}{4-K}$$

$$\Rightarrow RC = \frac{\sqrt{2}}{\omega_0}, \quad K = 4 - \sqrt{2}/Q, \quad R_B = (K-1)R_A$$

④ Example 3.13

* Band-reject KRC filter

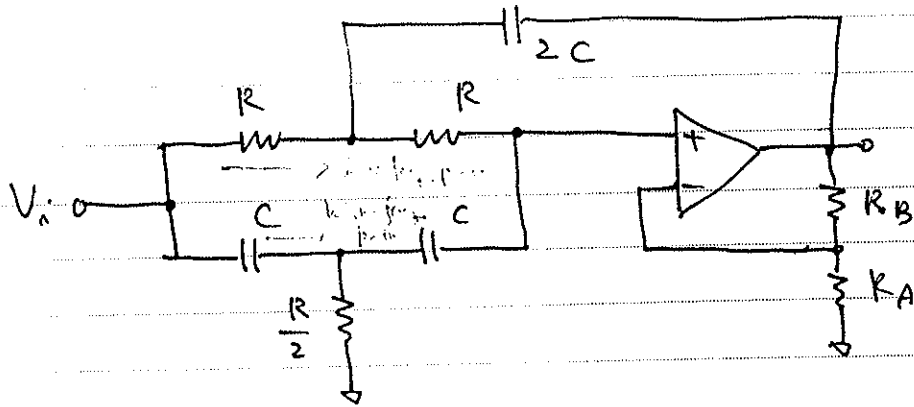


C Twin-T network

$$H_{0dB} = K, \quad \omega_0 = \frac{1}{RC}, \quad \beta = \frac{1}{4-K}$$

Example 3.14

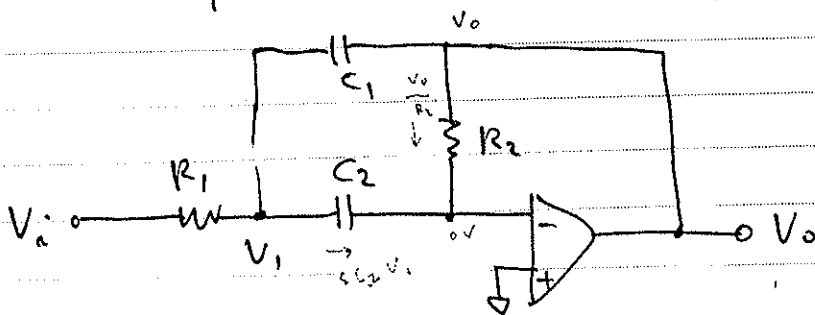3.6 Multiple feedback filters

* Band-pass filter (Delyiannis - Friend filter)



$$V_o = -s R_2 C_2 V_1 \quad (\text{KCL at negative input}) \quad \frac{V_o}{R_2} + \frac{V_1}{sC_1} = 0$$

$$\frac{V_i - V_1}{R_1} + \frac{V_o - V_1}{1/sC_1} + \frac{0 - V_1}{1/sC_2} = 0$$

$$H(j\omega) = \frac{-j\omega R_2 C_2}{1 - \omega^2 R_1 R_2 C_1 C_2 + j\omega R_1 (C_1 + C_2)}$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad \theta = \frac{\sqrt{R_2/R_1}}{\sqrt{C_1/C_2} + \sqrt{C_2/C_1}}$$

$$H_{0BP} = \frac{-R_2/R_1}{1 + C_1/C_2}$$

특정 조건


$$C_1 = C_2 = C$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2} C}, \quad \theta = 0.5 \sqrt{\frac{R_2}{R_1}}, \quad H_{0BP} = -2\theta^2$$

⇒

$$R_1 = \frac{1}{2\omega_0 \theta C}, \quad R_2 = \frac{2\theta}{\omega_0 C}$$


① $H_0 < 2\theta^2$ - 이 경우 θ 는

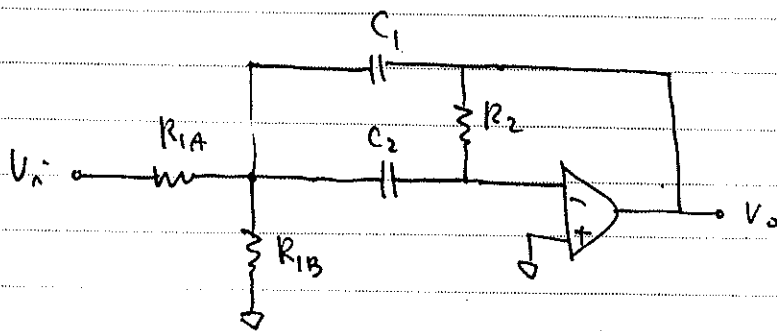

$$R_{1A} = \frac{\theta}{H_0 \omega_0 C}, \quad R_{1B} = \frac{R_{1A}}{\frac{2\theta^2}{H_0} - 1}$$

② Example 7.15

* Low-pass filter

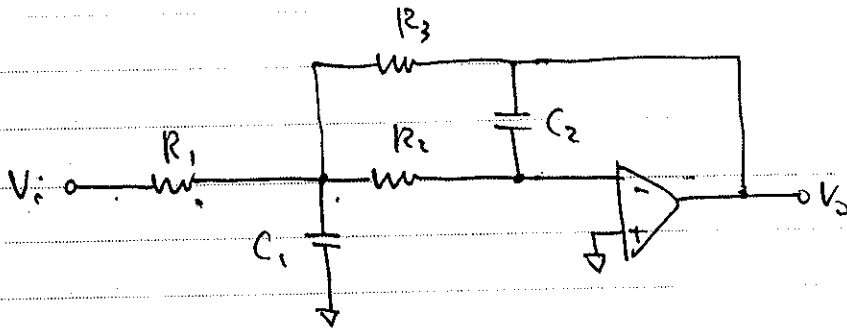

$$H_{OVP} = -\frac{R_3}{R_1} \quad \omega_0 = \frac{1}{\sqrt{R_2 R_3 C_1 C_2}}$$

$$\theta = \frac{1}{\sqrt{\frac{R_2 R_3}{R_1^2} + \sqrt{\frac{R_3}{R_2}} + \sqrt{\frac{R_2}{R_3}}}}$$

$$\begin{cases} R_3 \gg \omega_0^2 \Rightarrow \omega_0 \approx \frac{1}{\sqrt{R_2 R_3}} \\ R_1 \gg \omega_0^2 \Rightarrow \theta \approx \frac{1}{\sqrt{\frac{R_2}{R_3}}} \end{cases}$$


Design

- ① $C_2 \approx \frac{1}{\omega_0^2 R_3}$
- ② $C_1 = n C_2$ with $n \geq 4\theta^2 (1+H_0)$
- ③ $R_3 = \frac{1 + \sqrt{1 - 4\theta^2 (1+H_0)/n}}{2\omega_0 \theta C_2}$
- $R_1 = \frac{R_3}{H_0}$
- $R_2 = \frac{1}{\omega_0^2 R_3 C_1 C_2}$

Design:
 If ω_0 is too low \Rightarrow cap. value is too large
 \Rightarrow cap. value is too large \Rightarrow cap. value is too large
 greater spread
 Cap

② Example 3.16

* Notch filter

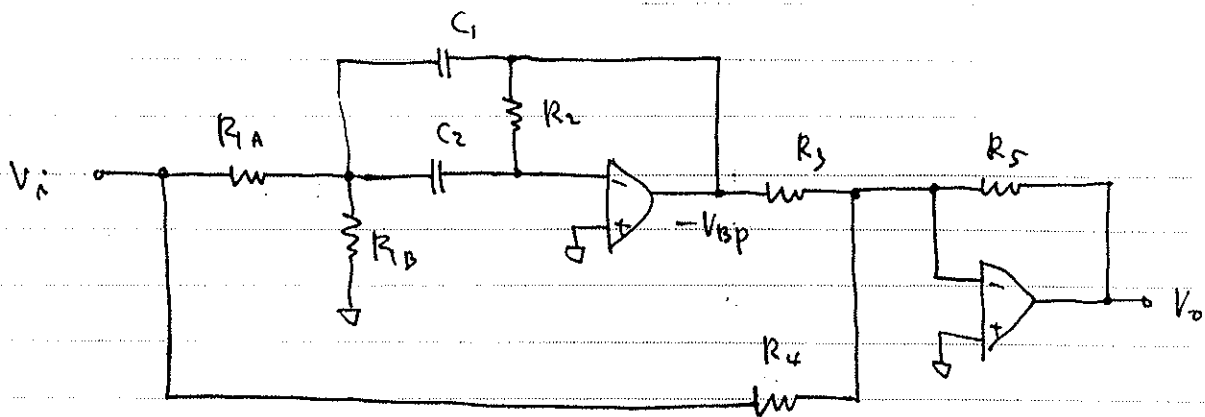

$$\frac{H_o R_4}{R_3} = 1 \Rightarrow \begin{cases} H(j\omega) = H_{on} H_n(j\omega) \\ H_{on} = -\frac{R_5}{R_4} \end{cases}$$

© Example 3.17

3.7 State-Variable and Biquad Filters

- multiple op amps
- easier to tune
- less sensitive to passive component values
- less component spreads
- more than one response (universal filter)

State-Variable Filter

- two op

- two


- two

- two

- two

... (continued from previous page)

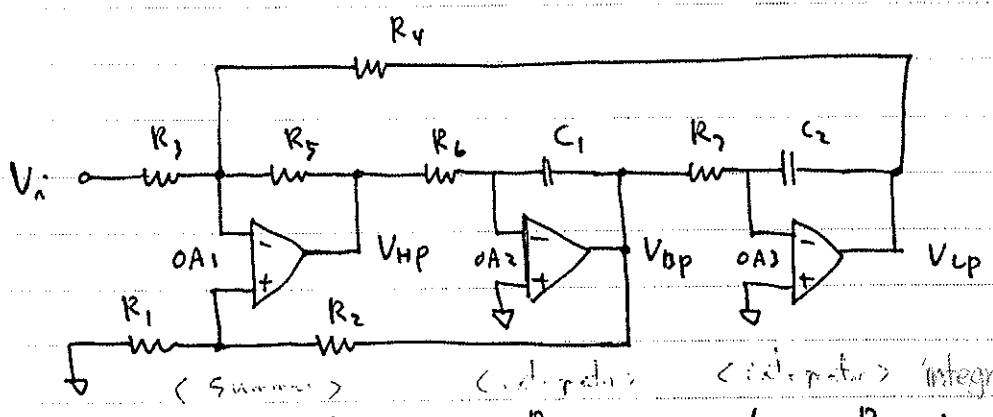- * State-Variable (SV) filters Hudman-Newcomb
 - KHN filters (Kerwin-Huels-Newcomb)
 - Two integrator and one summer
 - ⇒ 2nd order LPF, BPF, HPF
 - Op amp 1m ≈ 20 ⇒ notch, all-pass



$$\rightarrow V_{HP} = -\frac{R_5}{R_3} V_i - \frac{R_5}{R_4} V_{LP} + \left(1 + \frac{R_5}{R_3 \parallel R_4}\right) \frac{R_1}{R_1 + R_2} V_{BP}$$

$\frac{R_3 \parallel R_4}{R_3 R_4} = \frac{R_3 + R_4}{R_3 R_4}$

$$= -\frac{R_5}{R_3} V_i - \frac{R_5}{R_4} V_{LP} + \frac{1 + R_5/R_3 + R_5/R_4}{1 + R_2/R_1} V_{BP}$$

$$V_{BP} = \frac{-1}{R_6 C_1 s} V_{HP}$$

$$V_{LP} = \frac{-1}{R_7 C_2 s} V_{BP}$$

$$\left. \begin{matrix} V_{BP} = \frac{-1}{R_6 C_1 s} V_{HP} \\ V_{LP} = \frac{-1}{R_7 C_2 s} V_{BP} \end{matrix} \right\} \Rightarrow V_{LP} = \frac{1}{R_6 C_1 R_7 C_2 s^2} V_{HP}$$

plus full eq.

$$\textcircled{1} \frac{V_{HP}}{V_i} = H_{OHF} H_{HP} \quad \text{w/m}$$

$$H_{OHF} = -\frac{R_5}{R_3}$$

$$\omega_0 = \frac{\sqrt{R_5/R_4}}{\sqrt{R_6 C_1 R_7 C_2}}$$

$$Q = \frac{(1 + R_2/R_1) \sqrt{R_5 R_6 C_1 / R_4 R_7 C_2}}{1 + R_5/R_3 + R_5/R_4}$$

$$\textcircled{2} \quad \frac{V_{BP}}{V_i} = - \frac{1}{R_6 C_1 s} \frac{V_{HP}}{V_i} = H_{OHP} H_{BP}$$

$$H_{OHP} = - \frac{R_5}{R_3} \quad H_{BP} = \frac{1 + R_2/R_1}{1 + R_3/R_4 + R_3/R_5}$$

$$\textcircled{3} \quad \frac{V_{LP}}{V_i} = - \frac{1}{R_7 C_2 s} \frac{V_{BP}}{V_i} = H_{OHP} H_{LP}$$

$$H_{OHP} = - \frac{R_4}{R_3}$$

$$\text{조건: } \begin{cases} \theta \sim \frac{1}{\sqrt{2}} \\ \theta \approx \frac{1}{\sqrt{2}} \end{cases}$$

조건: $\left\{ \begin{array}{l} \text{metal-film resistor } \mu\text{g} \\ \text{poly styrene } \mu\text{g} \text{ poly carbonate cap. } \mu\text{g} \\ \text{op amp. or } \mu\text{g} \text{ m. bypass cap. } \mu\text{g} \end{array} \right.$

$$\text{조건: } R_5 = R_4 = R_3, \quad R_6 = R_7 = R$$

$$C_1 = C_2 = C$$

$$\Rightarrow \omega_0 = \frac{1}{RC}, \quad \theta = \frac{1}{3} \left(1 + \frac{R_2}{R_1} \right)$$

$$H_{OHP} = -1, \quad H_{BP} = \theta, \quad H_{LP} = -1$$

Tuning:
 ① Adjust R_4/R_3 with R_3 for gain
 ② Adjust R_3 for ω_0
 ③ Adjust R_2/R_1 for θ


⊙ Example 3.18

V_{i2} : ① R_3 output voltage divider ω_{LP}
 (ω_{LP} or dynamic range $\frac{1}{\omega_{LP}}$)

② Noninverting (Fig. 9.34) ω_{HP}
 $\omega_0 = \frac{1}{R_4 C_1}$, $Q = 1 + \frac{R_2}{2R_1}$

$$H_{OHP} = \frac{1}{Q} , H_{OBP} = -1 , H_{OLP} = \frac{1}{Q}$$

* Biquad filter (Tow-Thomas filter)

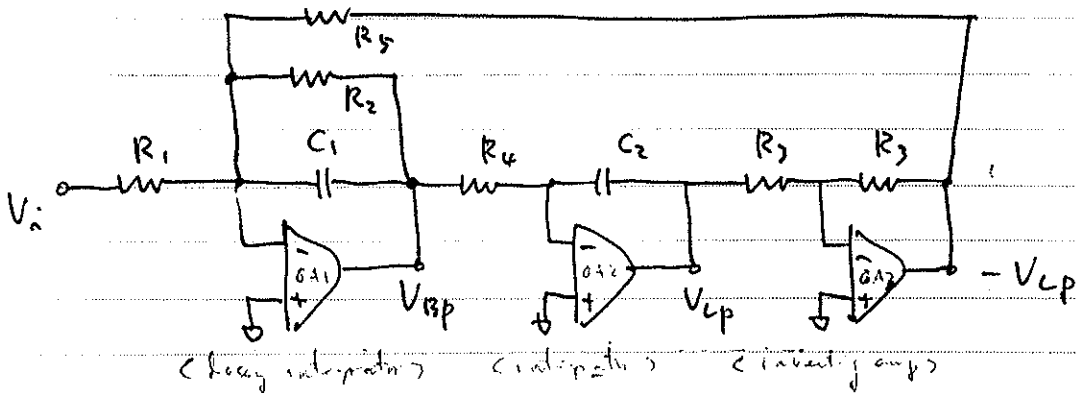

$$\left\{ \begin{aligned} \frac{V_i}{R_1} + \frac{-V_{LP}}{R_5} + \frac{V_{BP}}{R_2} + \frac{V_{BP}}{1/sC_1} &= 0 \\ V_{LP} &= -\frac{1}{sR_4C_2} V_{BP} \end{aligned} \right.$$

$$\Rightarrow \left\{ \begin{aligned} \frac{V_{BP}}{V_i} &= H_{OBP} H_{BP} \\ \frac{V_{LP}}{V_i} &= -\frac{1}{sR_4C_2} \frac{V_{BP}}{V_i} = H_{OLP} H_{BP} \end{aligned} \right.$$

$$H_{OBP} = -\frac{R_2}{R_1} , H_{OLP} = \frac{R_5}{R_1} , \omega_0 = \frac{1}{\sqrt{R_4 R_5 C_1 C_2}}$$

* HP response is $\frac{R_2}{R_1}$
 * common mode $\frac{R_2}{R_1}$ (HP response $\rightarrow \frac{R_2}{R_1}$)

$$\theta = \frac{R_2 \sqrt{C_1}}{\sqrt{R_4 R_5 C_2}}$$

2nd: $R_4 = R_5 = R, C_1 = C_2 = C$

$$H_{0BP} = -\frac{R_2}{R_1}, H_{0LP} = \frac{R}{R_1}$$

$$\omega_0 = \frac{1}{R_1 C}, \theta = \frac{R_2}{R}$$

- Tuning:
- ① Adjust R_4 and R_5 for ω_0
 - ② Adjust R_2 for θ
 - ③ Adjust R_1 for H_{0BP} and H_{0LP}

① Example 3.19

* Notch Response

72: [SV + op amp] 2nd [Biquad + op amp]

3rd: 2nd 3.37

$$V_N = - \left[\frac{R_5}{R_2} (V_i - V_{BP}) + \frac{R_5}{R_4} V_{LP} \right]$$

$$\frac{V_N}{V_i} = - \frac{R_5 \omega_z^2}{R_2 \omega_0^2} \frac{1 - (\omega/\omega_z)^2}{1 - (\omega/\omega_0)^2 + (j\omega/\omega_0)/\theta}$$

$$\omega_0 = \frac{1}{R_1 C}, \theta = \frac{R_1}{R}, \omega_z = \omega_0 \sqrt{1 \pm R_2/R_4}$$

↳ notch freq.

기) 7.21 기) 7.21

① $R_4 \approx \infty$ ($R_4 = \infty$)

$$\omega_z = \omega_0, \quad H_{0N} = -\frac{R_5}{R_2}$$

\Rightarrow symmetric notch (2.21 3.38 (b))

② $S(\omega) \approx \frac{\omega^2}{1 + \frac{R_2}{R_4 Q}}$

$$\omega_z = \omega_0 \sqrt{1 + \frac{R_2}{R_4 Q}}, \quad H_{0HP} = -\frac{R_5 \omega_z^2}{R_2 \omega_0^2}$$

($\omega_z > \omega_0$)

dc gain

$$H_{0HP} = -\frac{R_5}{R_2}$$

\Rightarrow low-pass notch (2.21 3.38 (a))

③ $S(\omega) \approx \frac{\omega^2}{1 - \frac{R_2}{R_4 Q}}$

$$\omega_z = \omega_0 \sqrt{1 - \frac{R_2}{R_4 Q}}, \quad H_{0HP} = -\frac{R_5}{R_2}$$

($\omega_z < \omega_0$)

high-freq. gain

$$H_{0HP} = -\frac{R_5 \omega_z^2}{R_2 \omega_0^2}$$

\Rightarrow high-pass notch (2.21 3.38 (c))

기) : $R = \frac{1}{\omega_0 C}, \quad R_1 = QR, \quad R_4 = \frac{R_2 \omega_0^2}{\omega_0^2 - \omega_z^2}$

$R_5 = R_2 \left(\frac{\omega_0}{\omega_z}\right)^2$ for $\omega_z > \omega_0$

$R_5 = R_2$ for $\omega_z < \omega_0$

④ Example 3.20

3.8 Sensitivity

$$S_x^y = \frac{\partial y / y}{\partial x / x} = \frac{x}{y} \frac{\partial y}{\partial x}$$

$$\Rightarrow \frac{\Delta y}{y} \approx S_x^y \frac{\Delta x}{x} \quad \text{for small } \Delta x$$

$\underbrace{\quad}_{\text{fractional parameter change}}$
 $\underbrace{\quad}_{\text{fractional component change}}$

$$\left. \begin{aligned}
 S_x^{1/x} &= S_x^{1/y} = -S_x^y \\
 S_x^{y_1 y_2} &= S_x^{y_1} + S_x^{y_2} \\
 S_x^{y_1 / y_2} &= S_x^{y_1} - S_x^{y_2} \\
 S_x^{x^n} &= n \\
 S_{x_1}^y &= S_{x_2}^y S_{x_1}^{x_2}
 \end{aligned} \right\}$$

* KRC Filter Sensitivities

For LP KRC filter (Fig 3.23),

$$\omega_0 = \frac{1}{\sqrt{R_1 C_1 R_2 C_2}}$$

$$S_{R_1}^{\omega_0} = S_{C_1}^{\omega_0} = S_{R_2}^{\omega_0} = S_{C_2}^{\omega_0} = -\frac{1}{2}$$

$\frac{\Delta \omega_0}{\omega_0} \approx \frac{1}{2} \left(\frac{\Delta R_1}{R_1} + \frac{\Delta C_1}{C_1} + \frac{\Delta R_2}{R_2} + \frac{\Delta C_2}{C_2} \right)$

{ Equal component design $\Rightarrow S_x^{\omega} \uparrow$ as $Q \uparrow$
 { Unity gain design \Rightarrow lower S_x^{ω}

© Example 3.21

* Multiple Feedback Filter Sensitivities

$\frac{\partial \omega_c}{\partial R_1} = \frac{\partial \omega_c}{\partial R_2} = \frac{\partial \omega_c}{\partial R_3} = 3.30$
 \Rightarrow Sensitivity $\approx \frac{\partial \omega_c}{\omega_c} = 1\% (3.97 - 3.98)$

* Multiple Op Amp Filter Sensitivities

- Biquad filter in Fig 3.26 : $0.1\% \text{ sensitivity}$
 \rightarrow low sensitivity

- SV filter : $0.1\% \text{ sensitivity}$
 \Rightarrow low sensitivity.