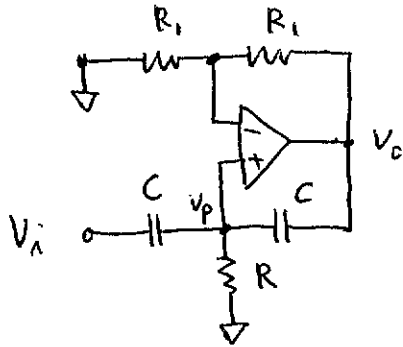


3 장 5 제 해답

3-2



$$(a) \begin{cases} \frac{V_i - V_p}{1/sC} = \frac{V_p}{R} + \frac{V_p - V_o}{1/sC} \\ \frac{V_p}{R_i} = \frac{V_o - V_p}{R_i} \end{cases} \Rightarrow V_p = \frac{1}{2} V_o$$

$$sC(V_i - sC V_p) - \frac{V_p}{R} - sC V_p = -sC V_o$$

$$sC V_i = 2sC V_p + \frac{V_p}{R} - sC V_o$$

$$= \frac{V_o}{2R}$$

$$\therefore H(s) = \frac{V_o}{V_i} = s2RC \quad ; \quad \text{비반전 미분기}$$


$$(b) H(j\omega) = j\omega 2RC$$

$$\omega = 2\pi \times 100 \text{ 라디안} \quad |H(j\omega)| = 1 \quad \text{이므로}$$

$$2\pi \times 100 \times 2RC = 1 \Rightarrow RC = \frac{1}{400\pi} \approx 8 \times 10^{-4}$$

$$C = 0.1 \mu\text{F}, \quad R = 800 \text{ k}\Omega$$

3-3

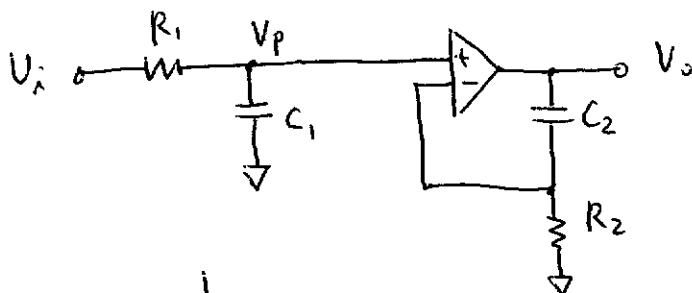

$$\text{단, } R_1 C_1 = R_2 C_2$$

$$(a) V_p = \frac{1}{1 + sR_1 C_1} V_i$$

$$V_o = \left(1 + \frac{1/sC_2}{R_2} \right) V_p = \left(1 + \frac{1}{sR_2 C_2} \right) \frac{1}{1 + sR_1 C_1} V_i$$

$$= \frac{1}{sR_2 C_2} V_i$$

$$\therefore H(s) = \frac{V_o}{V_i} = \frac{1}{sR_2C_2} \quad : \text{비반전 적분기}$$


$$(b) H(j\omega) = \frac{1}{j\omega R_2 C_2}$$

$$\omega = 2\pi \times 100 \text{ rad/s} \quad |H|_{dB} = 20 \log_{10} \frac{1}{2\pi \times 100 R_2 C_2} = 20$$

$$R_2 C_2 = \frac{1}{2000\pi} \doteq 1.6 \times 10^{-4}$$

$$C_2 = C_1 = 0.1 \mu\text{F}, \quad R_2 = R_1 = 1.6 \text{ k}\Omega$$

3-10

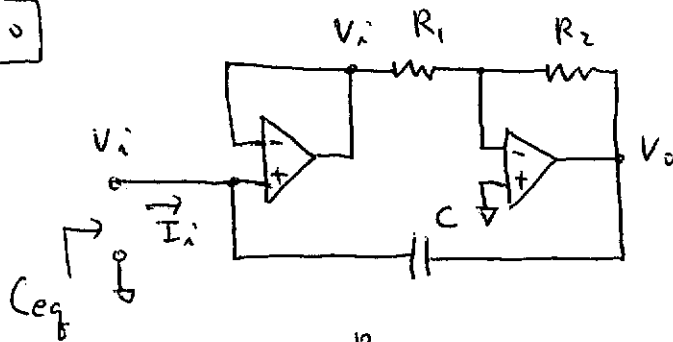

$$(a) \quad V_o = -\frac{R_2}{R_1} V_i$$

$$I_i = \frac{V_i - V_o}{1/sC} = \frac{(1 + \frac{R_2}{R_1}) V_i}{1/sC} = sC \left(1 + \frac{R_2}{R_1}\right) V_i$$

$$\therefore C_{eq} = C \left(1 + \frac{R_2}{R_1}\right)$$

$$(b) \quad C = 0.1 \mu\text{F}$$

$$R_2 = 1 \text{ M}\Omega \text{ pot.}$$

$$R_2 = 0 \text{ } \frac{1}{2} \text{ cm} \quad C_{eq} = 0.1 \mu\text{F}$$


$$R_2 = 1 \text{ M}\Omega \text{ } \frac{1}{2} \text{ cm} \quad C_{eq} = 0.1 \times \left(1 + \frac{1000}{R_1}\right) = 100$$

$$R_1 = \frac{1000}{999} \doteq 1 \text{ k}\Omega$$

3-19

HP KRC Filter
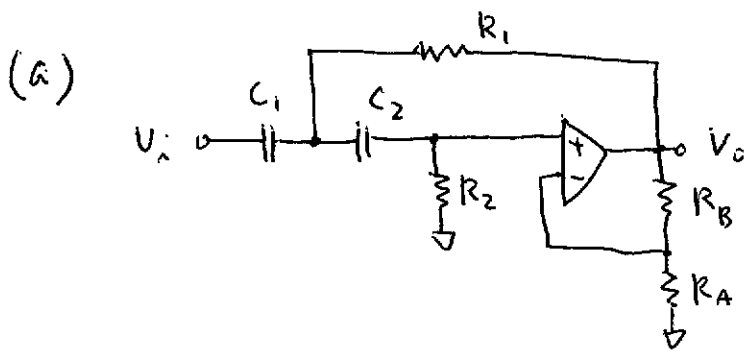
$$f_0 = 100 \text{ Hz}, \quad Q = 0.5 \sim 5 \text{ with } 100 \text{ k}\Omega \text{ pot.}$$



Equal component design 이 용도 하기

$$R_1 = R_2 = R, \quad C_1 = C_2 = C$$

$$\omega_0 = \frac{1}{RC} = 2\pi \times 100 \Rightarrow RC \doteq 1.6 \times 10^{-3}$$

$$C = 0.1 \mu\text{F}, \quad R = 16 \text{ k}\Omega$$

$$K = 3 - \frac{1}{\theta} \text{ 이기 } 1 \leq K \leq 2.8$$


$$K = 1 + \frac{R_B}{R_A} \text{ 이기 } R_B \leq 100 \text{ k}\Omega \text{ pot.}$$

$$R_B = 0 \text{ 일 때 } K = 1$$

$$R_B = 100 \text{ k}\Omega \text{ 일 때 } 1 + \frac{100}{R_A} = 2.8 \text{ 이기}$$

$$R_A = 58.8 \text{ k}\Omega$$

(b) V_i : 60 Hz, 5 V_{rms}, 3V dc offset

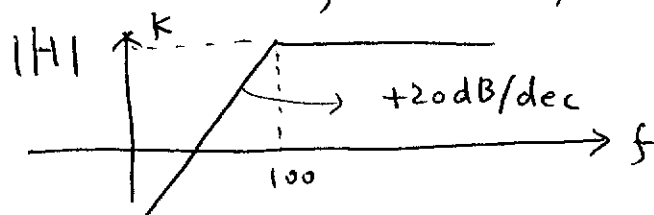

$$\frac{2\pi \times 60}{10} \text{ 가 } \frac{1}{10} \text{ 이면 } \frac{1}{2} \text{ 이 } \frac{1}{10} \text{ 이 됨.}$$


$$\text{따라서 } \frac{2\pi \times 60}{100} = \frac{6}{10} \text{ 이면 } \frac{1}{2} \text{ 이 } \frac{6}{10} \text{ 가 됨.}$$

$$\textcircled{1} K = 1 \text{ 일 때 } V_o \text{ 는 } \frac{6}{10} \times 5 = 3 \text{ V}_{\text{rms}}$$

$$\textcircled{2} K = 2.8 \text{ 일 때 } V_o \text{ 는 } \frac{6}{10} \times 2.8 \times 5 = 8.4 \text{ V}_{\text{rms}}$$

3V dc offset 은 HPF 이기 제거 됨.

3-22

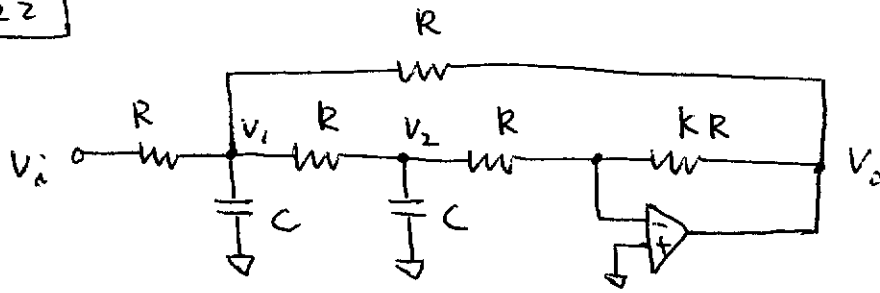

$$(a) \begin{cases} \frac{V_i - V_1}{R} = sC V_1 + \frac{V_1 - V_2}{R} + \frac{V_1 - V_o}{R} \\ \frac{V_1 - V_2}{R} = sC V_2 + \frac{V_2}{R} \\ \frac{V_2}{R} = -\frac{V_o}{kR} \Rightarrow V_o = -k V_2 \end{cases}$$

$$V_1 - V_2 = sCR V_2 + V_2 \Rightarrow V_1 = (2 + sCR) V_2 = -\frac{2 + sCR}{k} V_o$$

$$V_i - V_1 = sCR V_1 + V_1 - V_2 + V_1 - V_o$$

$$V_i = (3 + sCR) V_1 - V_2 - V_o$$

$$= -\left[\frac{(3 + sCR)(2 + sCR) - 1 + k}{k} \right] V_o$$

$$H(s) = \frac{V_o}{V_i} = \frac{-k}{(5 + k) + 5sCR + s^2 C^2 R^2}$$

$$H(j\omega) = \frac{-k}{5 + k} \frac{1}{1 + j\omega \frac{5}{5+k} RC - \omega^2 \frac{R^2 C^2}{5+k}}$$


$$\therefore Q = \frac{\sqrt{5+k}}{5}, \quad \omega_0 = \frac{\sqrt{5+k}}{RC}, \quad H_{OLP} = \frac{-k}{5+k}$$

$$(b) Q = 5 \text{ mHz}, \quad K = \sqrt{620} \doteq 24.9$$

$$\omega_0 = \frac{25}{RC} = 2\pi \times 2 \times 10^3 \text{ mHz}, \quad RC = 1.99 \times 10^{-3}$$

$$C = 0.1 \mu\text{F}, \quad R = 19.9 \text{ k}\Omega$$

3-27

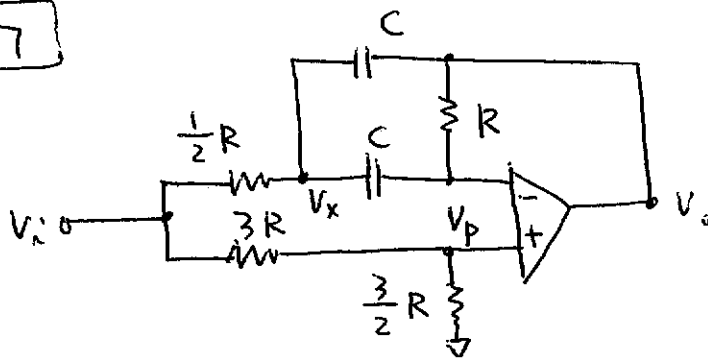

$$\left\{ \begin{aligned} V_p &= \frac{1}{3} V_i \\ \frac{V_i - V_x}{R/2} &= sC(V_x - V_p) + sC(V_x - V_o) \\ sC(V_x - V_p) &= \frac{V_p - V_o}{R} \end{aligned} \right.$$

$$\begin{aligned} sRC V_x &= (sRC + 1)V_p - V_o \\ &= \frac{1}{3}(1 + sRC)V_i - V_o \end{aligned}$$

$$V_x = \frac{1 + sRC}{3sRC} V_i - \frac{V_o}{sRC}$$

$$2V_i - 2V_x = sRC V_x - sRC V_p + sRC V_x - sRC V_o$$

$$\begin{aligned} \left(2 + \frac{sRC}{3}\right) V_i &= (2 + 2sRC)V_x - sRC V_o \\ &= \frac{2(1 + sRC)^2}{3sRC} V_i - \frac{2(1 + sRC)}{sRC} V_o - sRC V_o \end{aligned}$$


$$H(s) = \frac{V_o}{V_i} = \frac{1}{3} \frac{2 - 2sRC + s^2 R^2 C^2}{2 + 2sRC + s^2 R^2 C^2}$$

$$H(j\omega) = \frac{1}{3} \frac{1 - j\omega RC - \omega^2 \frac{R^2 C^2}{2}}{1 + j\omega RC - \omega^2 \frac{R^2 C^2}{2}}$$

$$\therefore H_{OAP} = \frac{1}{3}, \quad \omega_0 = \frac{\sqrt{2}}{RC}, \quad \theta = \frac{1}{\sqrt{2}}$$

3-31

(a)

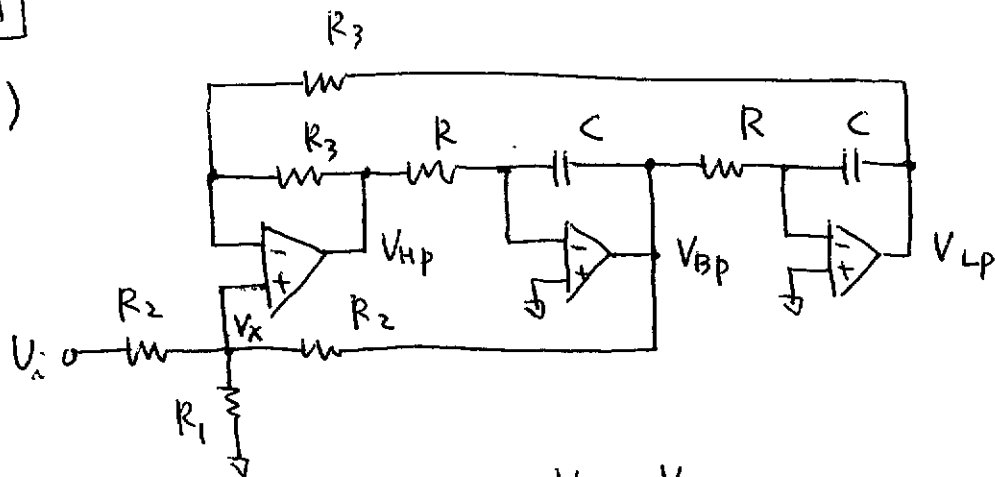

$$\frac{V_i - V_x}{R_2} = \frac{V_x}{R_1} + \frac{V_x - V_{BP}}{R_2}$$

$$\frac{V_x - V_{HP}}{R_3} = \frac{V_{HP}}{R} \Rightarrow V_x = \left(1 + \frac{R_3}{R}\right) V_{HP}$$

$$\frac{V_x - V_{HP}}{R_3} = \frac{V_{LP} - V_x}{R_3} \Rightarrow V_x = \frac{1}{2} (V_{HP} + V_{LP})$$

$$\frac{V_{HP}}{R} = -sRC V_{BP} \Rightarrow V_{HP} = -sRC V_{BP}$$

$$\frac{V_{BP}}{R} = -sRC V_{LP} \Rightarrow V_{BP} = -sRC V_{LP}$$

$$R_1 V_i - R_1 V_x = R_2 V_x + R_1 V_x - R_1 V_{BP} \quad \text{or } \Sigma \Sigma$$

$$V_i = \left(2 + \frac{R_2}{R_1}\right) V_x - V_{BP} \quad \Sigma \Sigma$$

$$V_{BP} = \left(2 + \frac{R_2}{R_1}\right) V_x - V_i$$

$$V_x = \frac{1}{2} (V_{HP} + V_{LP}) = \frac{1}{2} \left[-sRC V_{BP} - \frac{1}{sRC} V_{BP} \right]$$

$$= -\frac{1}{2} \frac{1 + s^2 R^2 C^2}{sRC} V_{BP}$$

$$V_{BP} = -\frac{1}{2} \left(2 + \frac{R_2}{R_1}\right) \frac{1 + s^2 R^2 C^2}{sRC} V_{BP} - V_i$$

$$\therefore V_i = - \left[\frac{sRC + \left(1 + \frac{R_2}{2R_1}\right) + \left(1 + \frac{R_2}{2R_1}\right) s^2 R^2 C^2}{sRC} \right] V_{BP}$$

$$H_{BP}(s) = \frac{V_{BP}}{V_i} = - \frac{sRC}{\left(1 + \frac{R_2}{2R_1}\right) + sRC + \left(1 + \frac{R_2}{2R_1}\right)s^2 R^2 C^2}$$

$$= - \frac{1}{1 + \frac{R_2}{2R_1}} \frac{sRC}{1 + s \frac{RC}{1 + \frac{R_2}{2R_1}} + s^2 R^2 C^2}$$

$$H_{BP}(j\omega) = - \frac{1}{1 + \frac{R_2}{2R_1}} \frac{j\omega RC}{1 + j\omega \frac{RC}{1 + \frac{R_2}{2R_1}} - \omega^2 R^2 C^2}$$

$$\therefore \omega_0 = \frac{1}{RC}, \quad Q = 1 + \frac{R_2}{2R_1}, \quad H_{0BP} = -1$$

$$H_{LP}(s) = - \frac{1}{sRC} H_{BP}(s) \quad \text{with} \quad H_{0LP} = \frac{1}{Q}$$

$$H_{HP}(s) = -sRC H_{BP}(s) \quad \text{with} \quad H_{0HP} = \frac{1}{Q}$$

(b) $f_L = 594 \text{ Hz}, \quad f_H = 606 \text{ Hz}$

$$f_0 = \sqrt{f_L f_H} \doteq 600 \text{ Hz}$$

$$RC = \frac{1}{2\pi \times 600} = 2.65 \times 10^{-4}$$

$$C = 0.1 \mu\text{F}, \quad R = 2.65 \text{ k}\Omega$$

$$Q = \frac{\omega_0}{BW} = \frac{600}{606 - 594} = 50 = 1 + \frac{R_2}{2R_1}$$

$$\frac{R_2}{R_1} = 98 \Rightarrow R_2 = 98 \text{ k}\Omega, \quad R_1 = 1 \text{ k}\Omega$$

$$R_3 \doteq 10 \text{ k}\Omega \quad \text{with}$$

(c) $H_{0LP} = \frac{1}{Q} = \frac{1}{50}$